

**CS 2102-01 Logic Design    Fall 2010    Midterm exam 1**  
**Sample Answers**

1.

(a) The main difference is the value continuity. Analog devices represent continuous value while digital devices represent discrete value. Note that the similar answers are also correct.

(b) Analog: 3, 4    Digital: 1, 2

2.

(a) 10010100110111

(b) 22467

(c) 10111001 10110101 00110010 00110111

3.

(a)  $f = A'C' + BC + ABC' + B'C' = C'(A' + AB + B') + BC = C'(A'(1+B) + AB + B') + BC = C'(A' + A'B + AB + B') + BC = C'(A' + (A' + A)B + B') + BC = C'(A' + B + B') + BC = C'(A' + 1) + BC = \underline{C' + BC}$

(b)(c)


AB \ C	0	1
00	1	0
01	1	1
11	1	1
10	1	0

*Simplest*  $f = C' + B$

(d)  $f(A, B, C) = \sum (0, 2, 3, 4, 6, 7) = \Pi(1, 5)$

4.

(a)

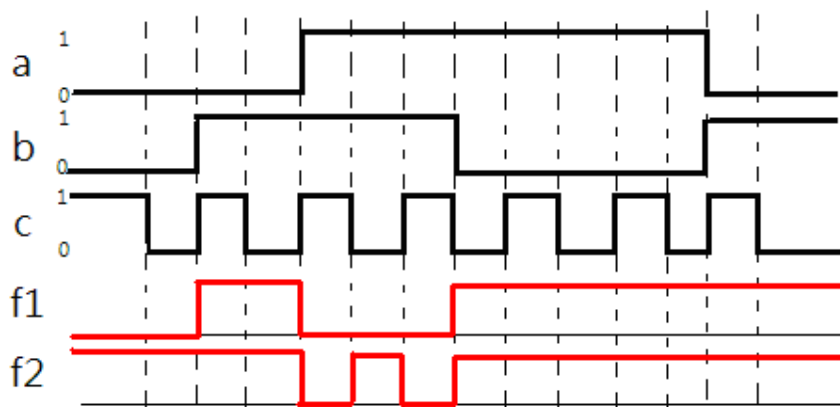


(b)

a	b	c	f1	f2
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	0	1
1	1	1	0	0

(c) f1: XOR f2: NAND


5.

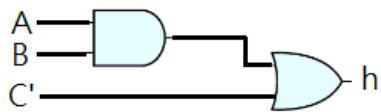(a) This sub-problem can use inverted signal.



(b)  $h' = (AB + C')' = (AB)'(C')' = (AB)'C = (A' + B')C$

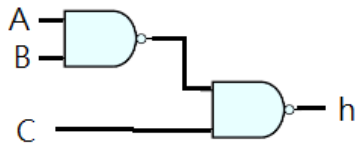(c) A NAND gate can be thought as  $(XY)'$ . Since  $h' = (A' + B')C = (AB)'C$ ,  $h = (h')' = ((AB)'C)'$  and hence two NAND gates.



6.

(a)

x	y	z	xyz	xz'	y'z	x'yz	$xyz + xz' + y'z + x'yz$	x+z
0	0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	1	1	1
1	0	0	0	1	0	0	1	1
1	0	1	0	0	1	0	1	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	1	1

By truth table, we can verify that  $f1 = f2$ .

(b)

$$xyz+xz'+y'z+x'yz$$

$$= (x+x')yz+xz'+y'z$$

$$= yz+xz'+y'z$$

$$= (y+y')z+xz'$$

$$= z+xz'$$

$$= z+xz+xz'$$

$$= z+(z+z')x$$

$$= z+x$$

$$= x+z$$

Hence,  $f1 = f2$ .

7.

(a) y

(b) x, f

(c) w, g