


# CS2101 Midterm I

1:20-3:00pm, Thursday, April 16, 2015


1. 10% Binary representations
  - i. Convert binary number  $010101_2$  to decimal number
  - ii. Represent decimal number  $1357_{10}$  in 12-bit binary number
  - iii. Represent decimal number  $-1357_{10}$  in 12-bit 2's complement binary number
2. 10% Prove that  $\sim(A \& B) = \sim A \mid \sim B$  /\* De Morgan's Theorem \*/
3. 20% In the K-Map below
  - i. Identify all prime implicants
  - ii. Identify all essential prime implicants
  - iii. Give a minimized Boolean expression of the function
  - iv. Implement the function using AND, OR and NOT gates

ab \ cd	00	01	11	10
00	1	0	1	1
01	0	0	1	0
11	0	1	1	0
10	1	X	1	1

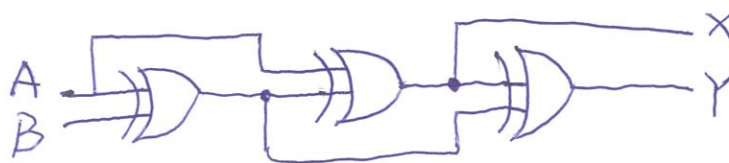
4. 10% Analyze the circuit schematic below. Express its function in Truth Table.



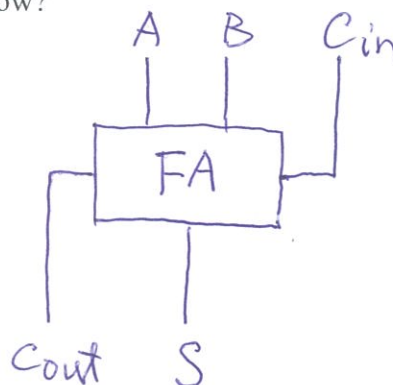
5. 10% We can implement a 1-bit full adder(FA) by composition of a majority function circuit and an odd function circuit.
  - i. Why?
  - ii. And How?



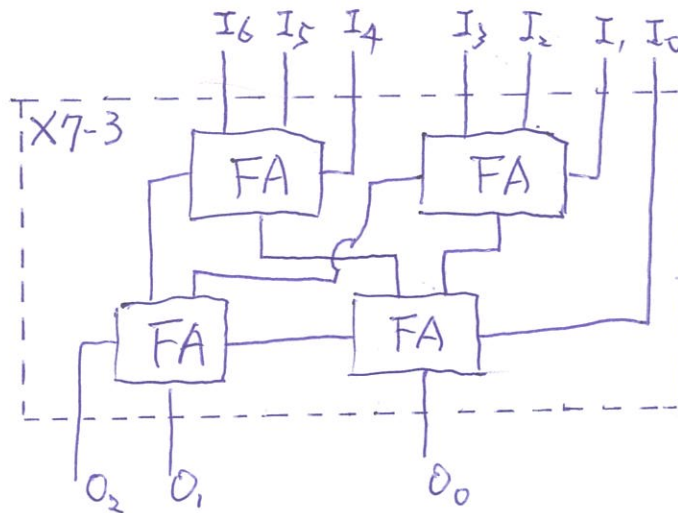6. 15% Below is a 7-input 3-output function called X7-3. Its input are vector of 7 bits and output 3-bit binary number.
- What is the function of X7-3?
  - Construct an X15-4 using X7-3s (and some additional FAs) as building blocks.



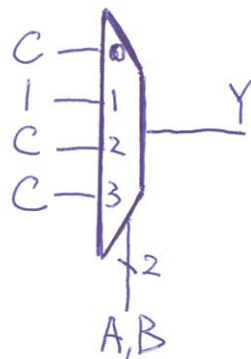7. 15% In addition to data selection, multiplexers can implement arbitrary function. Given a 4-to-1 multiplexer (binary select) below
- What is function  $Y = f(A, B, C)$ ?
  - Rewire the multiplexer to implement a 3-input NOR function.



8. 10% In an  $n$ -bit adder/subtractor circuit operating on 2's complement binary numbers, how is overflow detected?

1. <i><ii>  $010101_2 = 2^4 + 2^2 + 2^0 = 16 + 4 + 1 = 21_{10}$

<ii> 
$$\begin{array}{r} 2 \overline{) 1357} \\ \underline{2 \overline{) 678}} \dots 1 \\ \underline{2 \overline{) 339}} \dots 0 \\ \underline{2 \overline{) 169}} \dots 1 \\ \underline{2 \overline{) 84}} \dots 1 \\ \underline{2 \overline{) 42}} \dots 0 \\ \underline{2 \overline{) 21}} \dots 0 \\ \underline{2 \overline{) 10}} \dots 1 \\ \underline{2 \overline{) 5}} \dots 0 \\ \underline{2 \overline{) 2}} \dots 1 \\ 1 \dots 0 \end{array}$$

<iii>  $-1357_{10}$

$1357_{10} = 010101001101_2$

Verification

$$\begin{aligned} & 2^{10} + 2^8 + 2^6 + 2^3 + 2^2 + 2^0 \\ &= 1024 + 256 + 64 + 8 + 4 + 1 \\ &= 1357 \end{aligned}$$

1's Complement of  $010101001101$   
 $= 101010110010$


2's Complement  $= 101010110011$

2. Prove by Truth Table

A	B	A & B	$\sim(A \& B)$	$\sim A$	$\sim B$	$\sim A \& \sim B$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\sim(A \& B) = \sim A \& \sim B$

3.

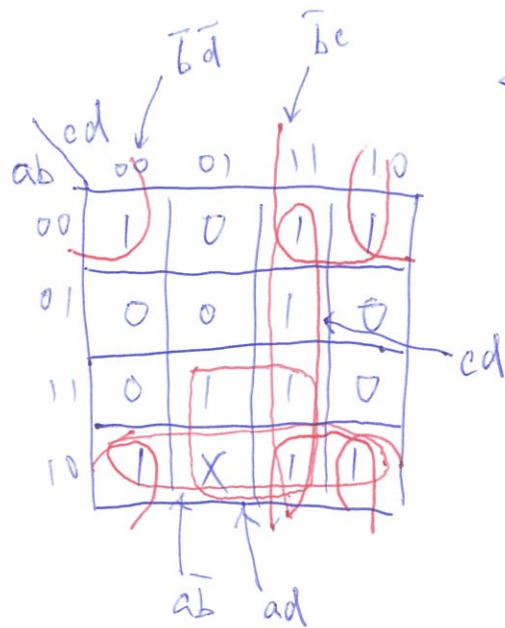

<i> Prime Implicants

$\bar{a}b, ad, cd, \bar{b}d, \bar{b}c$


<ii> Essential PI

$ad, cd, \bar{b}d$


<iii>

$$f = ad + cd + \bar{b}d$$

<iv>

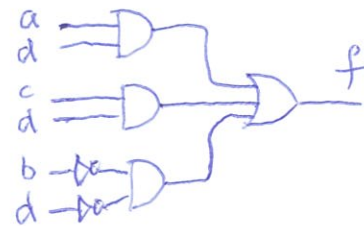

4.

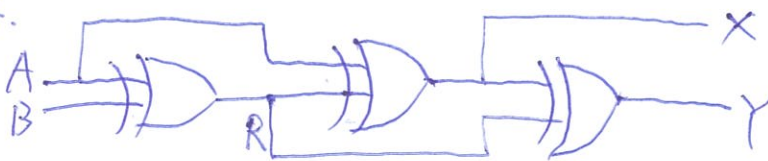

A	B	$R = A \oplus B$	$X = A \oplus R$	$Y = X \oplus R$
0	0	0	0	0
0	1	1	1	0
1	0	1	0	1
1	1	0	1	1

$$X = B$$

$$Y = A$$

This circuit SWAP two bits.


## 5. Full Adder

A	B	C <sub>in</sub>	cont.	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Why:

- Cont is 1 when two or more 1's is the input  
⇒ Majority Function
- S is 1 when one or three 1's is the input.  
⇒ ODD Function

How:

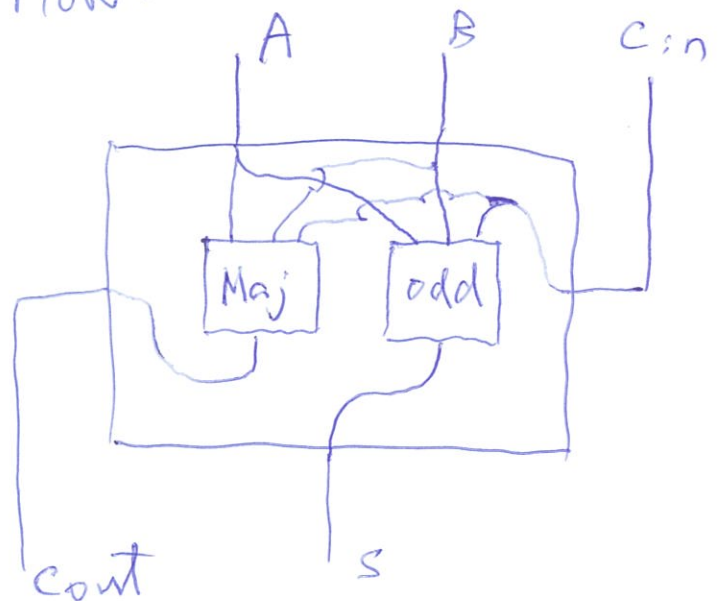

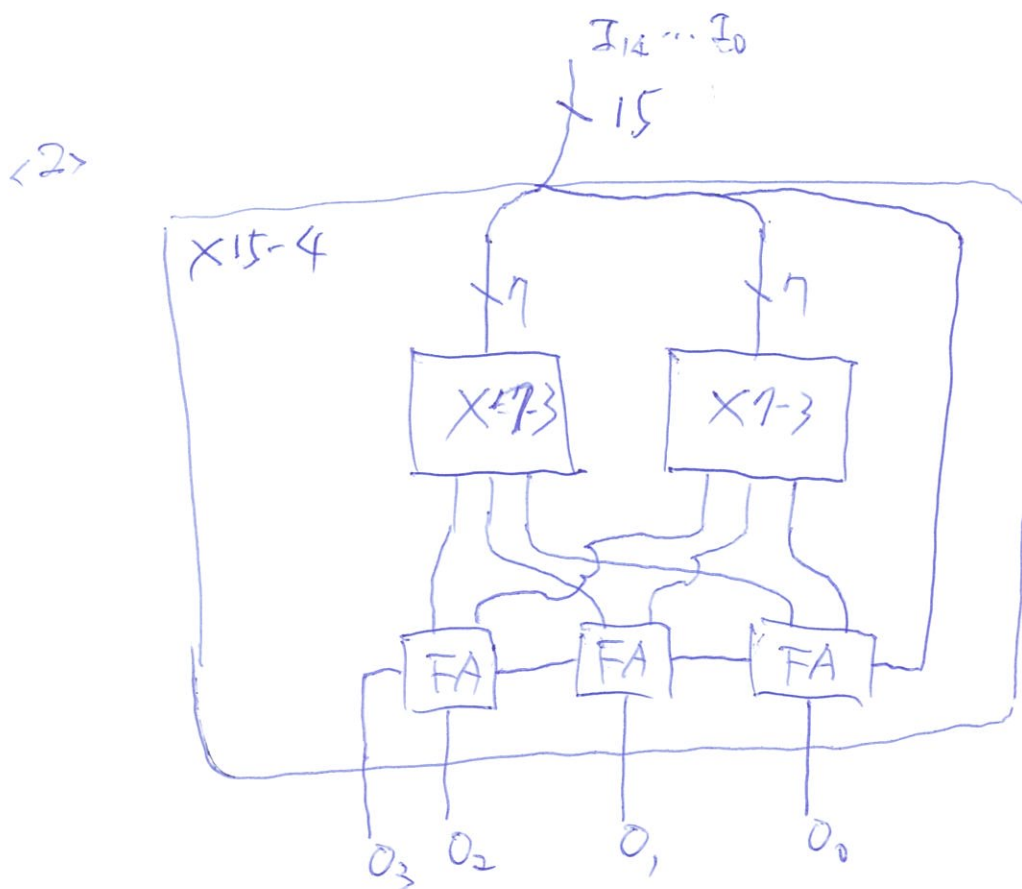6. <1> it counts number of 1's in the Input




7. <1>

A	B	C	Y	Y
0	0	0	C	0
0	0	1	C	1
0	1	0	1	1
0	1	1	1	1
1	0	0	C	0
1	0	1	C	1
1	1	0	C	0
1	1	1	C	1

<ii>


A	B	C	NOR(ABC)	
0	0	0	1	$\bar{C}$
0	0	1	0	
0	1	0	0	0
0	1	1	0	
1	0	0	0	0
1	0	1	0	
1	1	0	0	0
1	1	1	0	

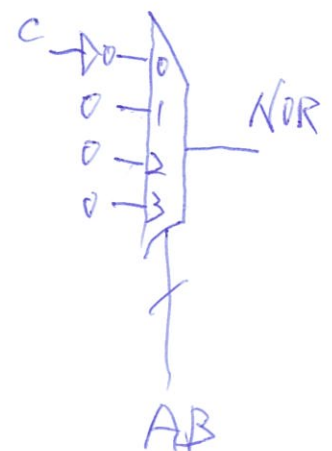

Y is a prime number detector



8.

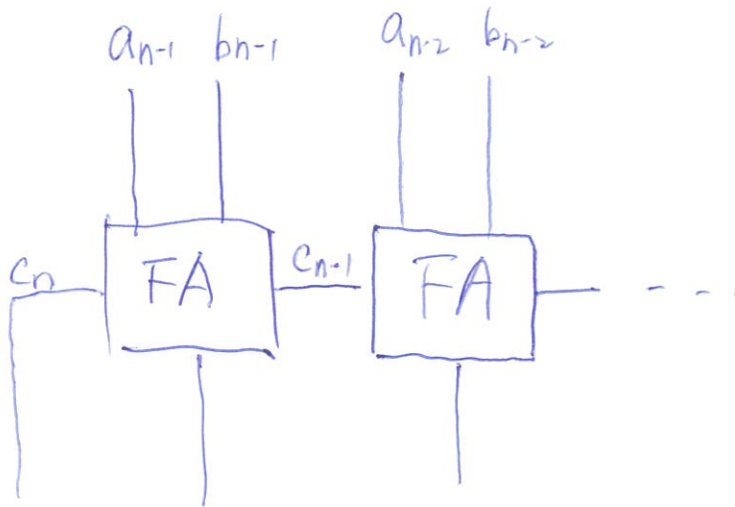

A	B	
+	-	No OVF
+	+	$a_{n-1}=0, b_{n-1}=0$ , OVF when $c_{n-1}=1, c_n=0$
-	-	$a_{n-1}=1, b_{n-1}=1$ , OVF when $c_{n-1}=0, c_n=1$
-	+	No OVF

$\Rightarrow$   
OVF detection ckt

