

Part I: Questions and answers (36%, 6% each)

1. Design a diode logic circuit which implements $F = a + bcd$.
2. State the reasons about the naming of MOSFETs.
3. What is "Hole Inversion Layer" and how to form it in a MOS?
4. Explain the Early Effect of a MOS.
5. Use diodes to design a Gate input protection circuit for a MOS such that the Gate voltage will be never greater than 10V. Assume the V_r of a diode is 0.6V when forward biased.
6. Use 10 MOSFETs to design a CMOS logic circuit which implements $F = (a' + b)c + d'e$. Assume the inverted inputs are allowed.

Part II: Choose a correct answer: (74%, 3% each except notified)

1. The so-called 45nm process in IC fabrication means the [(1) channel width (2) channel length (3) oxide thickness (4) none of the above] of MOS is greater than 45nm, or equal to 45nm.
2. The Early Effect is getting more important when the channel length of MOS is [(1) getting smaller (2) getting larger (3) unchanged (4) none of the above].
3. To [(1) decrease (2) increase (3) keep unchanged (4) none of the above] the V_{TN} of enhancement mode nMOS, C_{ox} has to be increased.
4. Which one is not the operation mode in the depletion mode pMOS? [(1) depletion mode (2) enhancement mode (3) linear mode (4) none of the above]

5. One way to make the threshold voltage of an enhancement nMOS smaller is to [(1) decrease (2) increase (3) keep unchanged (4) none of the above] the impurity concentration of p-type substrate.
6. The threshold voltage of an enhancement nMOS will [(1) increase (2) decrease (3) keep unchanged (4) none of the above] when the temperature increases.
7. (5%) Given an input waveform and a diode circuit as shown in Fig. 1 and Fig. 2, respectively. Determine the output waveform at V_o . (Assume the diode is an ideal diode, forward \rightarrow ON, reverse \rightarrow OFF).

 


Fig. 1 Input waveform



 


Fig. 2 Diode circuit


(1)

 


(2)

 

(3)

 

(4)

 

8. For the circuit in Fig. 3. (Assume the diodes have $V_r = 0.6V$ when forward biased)
- (a) What is the value of I_D ? [(1) 0mA (2) 1mA (3) 2mA (4) None of the above]
- (b) What is the value of V_o ? [(1) -7.5V (2) -5V (3) 4.4 V (4) None of the above]

 


Fig. 3

9. The mechanism that the depletion region around the drain terminal extends completely through the channel to the source terminal is called [(1) punch-through breakdown effect (2) body effect (3) Early effect (4) subthreshold conduction effect].
10. Given a pMOS with $V_{TP} = 2V$, $k_p = 0.5 \text{ mA/V}^2$ at Saturation region, what is the value of I_{DSS} ? [(1) 2mA (2) 4.5mA (3) 8mA (4) none of the above]
11. (5%) Given an input waveform and an output waveform as shown in Fig. 4 and Fig. 5, respectively. Determine the diode circuit. (Assume the diode is an ideal diode, forward \rightarrow ON, reverse \rightarrow OFF).

 


Fig. 4 Input waveform



 


Fig. 5 Output waveform


(1)

 


(2)

 

(3)

 

(4)

 

12. Consider the circuit in Fig. 6. The transistor parameters are $V_{TN} = 1V$, $k_n' = 50\mu A/V^2$.

- Design the width-to-length ratio required in M1 transistor such that $I_D = 0.64mA$, $V_1 = 2V$, and $V_2 = 5V$. [(1) 4/5 (2) 8/5 (3) 16/5 (4) 32/5]
- Design the width-to-length ratio required in M3 transistor such that $I_D = 0.64mA$, $V_1 = 2V$, and $V_2 = 5V$. [(1) 16/5 (2) 32/5 (3) 64/5 (4) 128/5]

 


Fig. 6

13. Consider an enhancement nMOS. Given $V_{TN} = 1V$, $k_n = 0.1mA/V^2$, $V_{GS} = 2V$, $V_A = 50V$, and $V_{DS} = 3V$.
- (a) Determine the output resistance (r_o). [(1) $125k\Omega$ (2) $166.7k\Omega$ (3) $500k\Omega$ (4) None of the above]
- (b) Determine the current I_D . [(1) $0.102mA$ (2) $0.106mA$ (3) $0.108mA$ (4) $0.11mA$]
14. Which of the following does not affect the value of threshold voltage of MOS? [(1) channel length (2) oxide permittivity (3) oxide thickness (4) substrate impurity concentration]
15. (5%) Consider the circuit in Fig. 7. The transistor parameters are $V_{TN} = 2V$, $k_n' = 20\mu A/V^2$, $L = 10\mu m$, $W = 400\mu m$. Design R_s such that $I_D = 0.4mA$. [(1) $2k\Omega$ (2) $5k\Omega$ (3) $7.5k\Omega$ (4) None of the above]

 


Fig. 7

16. For a MOS circuit as shown in Fig. 8. Given $V_{TN} = -1V$, $k_n' = 20\mu A/V^2$.
- (a) Determine the maximal value of R_D such that the MOS is at Saturation region and $I_D = 50\mu A$. [(1) $20k\Omega$ (2) $40k\Omega$ (3) $60k\Omega$ (4) $80k\Omega$]
- (b) Determine the minimal value of R_D such that the MOS is at Saturation region and $I_D = 50\mu A$. [(1) $30k\Omega$ () $40k\Omega$ () $50k\Omega$ (4) None of the above]

 


Fig. 8

17. What is the boundary equation between triode region and saturation region in nMOS? [(1) $I_D = k_n \times V_{DS}$ (2) $I_D = k_n \times (V_{GS} - V_{TN})^2$ (3) $I_D = k_n \times V_{DS}^2$ (4) $I_D = k_n \times V_{GS}^2$]
18. (5%) Given a CMOS logic circuit as shown in Fig. 9 where the nMOS network is not shown explicitly. What is the Boolean function of V_o ? (A' means the complement of A) (1) $A'B'E'+C'+D'F'$ (2) $A'B'E'+A'C'+A'D'F'$ (3) $(A(BE+C+DF))'$ (4) $A(BE+C+DF)$.

 


Fig. 9

Enjoy Your Summer Break !!

Thanks for your cooperation, looking forward to seeing you again in the future!