 


國立清華大學 電機工程學系  
九十五學年度 第一學期  
EE-2280 邏輯設計 期中考試題  
本試題 - 共計兩頁，七大題，總分 100 分  
Closed-Book Examination (考試日期: 11/7/2006)

1. (40%) Answer the following questions briefly.
  - (a) Calculate the *13's complement* of  $(ABBA)_{14}$ . Note that you answer should be in radix-14 notation. (5%)
  - (b) What is the *most negative number* that can be represented using 10-bit 2's complement integer representation? (5%)
  - (c) State the distinctive feature of the *Gray code* in one sentence. (5%)
  - (d) Will an addition operation  $(-3)+(2)$  yield an *end carry*? Assume that the 2's complement notation is used for representing the 4-bit signed integers. (Simply answer yes or no). (5%)
  - (e) How many output signals does a normal  $k$ -input decoder have? (5%)
  - (f) An *essential prime implicant* is a prime implicant containing an essential minterm. What is an *essential minterm*? Define it in one sentence. (5%)
  - (g) Express the function of the *sum bit*,  $S_i$ , of a full-adder cell in terms of its three inputs,  $A$ ,  $B$ ,  $C_{in}$ . (Feel free to use any primitive logic operator we ever discussed in class.) (5%)
  - (h) Express the *carry output bit* function  $C_{i+1}$  at a bit position of a binary adder in terms of the *carry input signal*  $C_i$ , its *carry propagate signal*  $P_i$ , and *carry generate signal*  $G_i$ . (5%)
2. (10%) Cover  $(3.4)_{10}$  to its unsigned binary format,  $(YY.XXXX)_2$ , where symbol 'X' or 'Y' is a binary bit.
  - (a) Show the binary code of "YY". (5%)
  - (b) Show the binary code of "XXXX". (5%)
3. (10%) Determine the base (or radix) of the numbers so that  $(54)/4 = (13)$ .
4. (10%) Minimize a function into its product-of-sum form,  $F(x, y, z) = x'y'z + x'yz + xyz$ .
5. (10%) Convert the following NOR-OR implementation into its equivalent All-NAND two-level implementation. Draw your logic circuit and mark each input clearly.



6. (10%) Draw a complete 4-bit adder/subtractor using full-adders (FA) and XOR gates as the building blocks. Let the two inputs be  $(A_3 A_2 A_1 A_0)$  and  $(B_3 B_2 B_1 B_0)$ . The circuit performs addition  $A+B$  when the mode select signal  $M=0$ , and subtraction  $A-B$  when  $M=1$ . Indicate your sum bits  $(S_3 S_2 S_1 S_0)$  and the overflow/underflow detection bit  $V$  clearly.

7. (10%) Consider the design of a 4-to-2 binary encoder.
- (a) Fill in the missing input combination in the following simplified truth table. (Note: impossible input combinations are ignored in a simplified truth table.) (5%)
- (b) Derive the Boolean expression of output function  $x$ . (5%)

Input ( $D_3D_2D_1D_0$ )	Output ( $x\ y$ )
0 0 0 1	0 0
0 0 1 0	0 1
0 1 0 0	1 0
(To be filled in)	1 1