
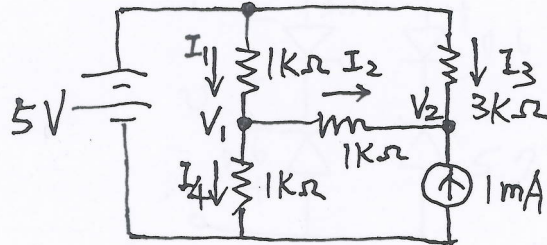


NOTE: 每一題都要寫出計算過程

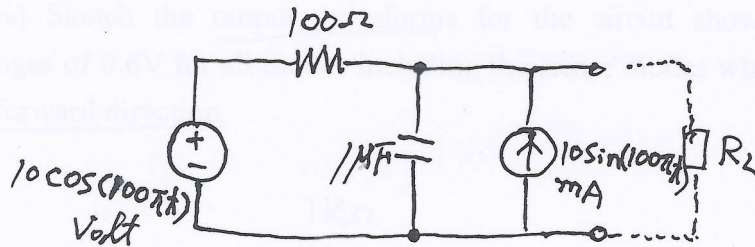1. (10%) Find  $V_1$ ,  $V_2$ ,  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$  using Node-Voltage Analysis.





2. (10%) Find the Thevenin equivalent circuit for the following circuit.




Voltage source:  
 $10\cos(100\pi t)$  volts  
 Current source:  
 $10\sin(100\pi t)$  mA

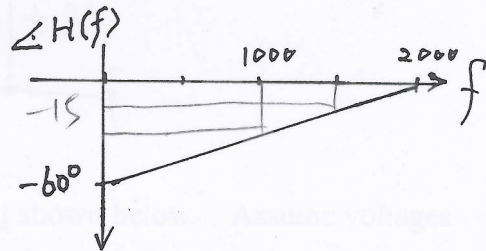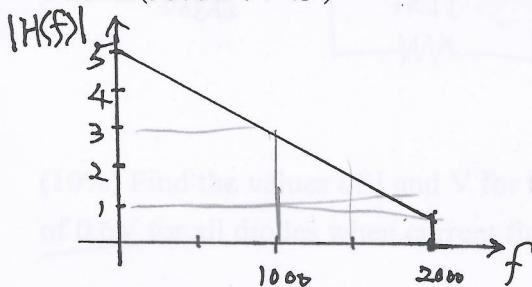3. (10%) A circuit is characterized by the following transfer function. Find its output  $v_{out}(t)$  for an input  $v_{in}(t) = 10 + 5\sin(2000\pi t + 30^\circ) + 10\cos(3000\pi t - 45^\circ) + 20\cos(5000\pi t + 45^\circ)$




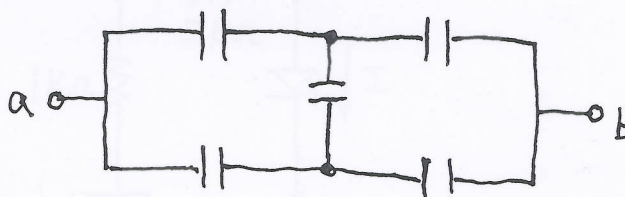4. (10%) Find equivalent capacitance  $C_{ab}$  for the following circuit assuming every capacitor is  $1\mu F$ .




$C_{ab} = 1\mu F$

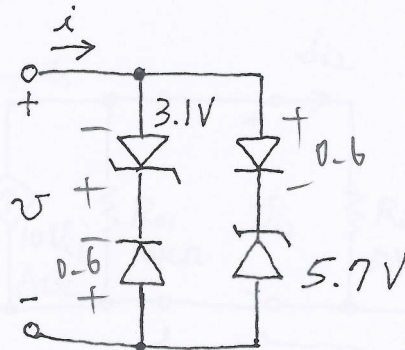
5. (10%) Sketch  $i$  versus  $v$  for the circuit shown below. Assume voltages of  $0.6V$  for all diodes including the Zener diodes when current flows in the forward direction.



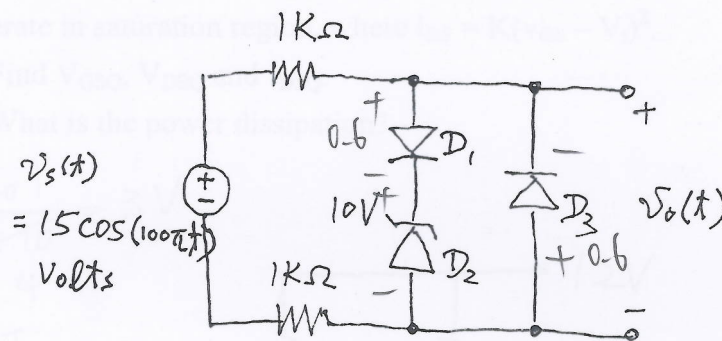6. (10%) Sketch the output waveforms for the circuit shown below. Assume voltages of  $0.6V$  for all diodes including the Zener diodes when current flows in the forward direction.



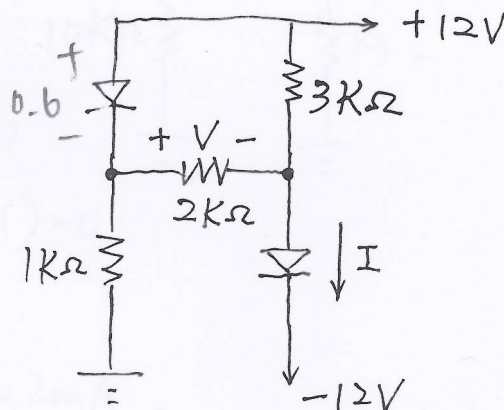7. (10%) Find the values of  $I$  and  $V$  for the circuit shown below. Assume voltages of  $0.6V$  for all diodes when current flows in the forward direction.




$$A_{isc} = A_{voc} \times \frac{R_i}{R_L} \Rightarrow A_{voc} = A_{isc} \times \frac{R_L}{R_i} = 10 \times \frac{5k}{1M}$$

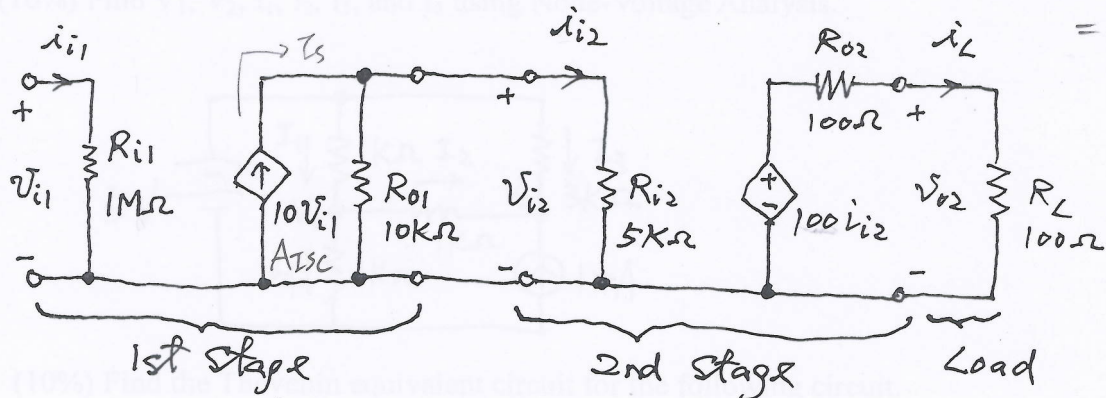8. (20%) Calculate voltage gain ( $A_v = v_{o2}/v_{i1}$ ), current gain ( $A_i = i_L/i_{i1}$ ) and power gain ( $A_p$  or  $G$ ) for the following two-stage cascaded amplifiers.

$$A_{v1} = \frac{10V_{i1} \times \frac{R_{o1}}{R_{o1} + R_{i2}} \times R_{i2}}{V_{i1}} = 10 \times \frac{50k \times 5k}{10k + 5k} = \frac{500k}{15}$$

$$A_{i1} = A_{v1} \times \frac{R_i}{R_L} = \frac{500k}{15} \times \frac{1M}{5k} = \frac{100M}{15}$$



$$A_{i2} = \frac{100i_{i2} \times \frac{1}{200}}{i_{i2}} = \frac{1}{2}$$

$$A_{v2} = A_{i2} \times \frac{R_L}{R_i} = \frac{1}{2} \times \frac{100 \times 50}{5k} = 10m$$

9. (20%) Assume the following N-type MOSFET has  $K = 2mA/V^2$ , and it is biased to operate in saturation region, where  $i_{DS} = K(v_{GS} - V_t)^2$ .

A. Find  $V_{GSQ}$ ,  $V_{DSQ}$  and  $I_{DSQ}$ .

B. What is the power dissipation?

$$V_t = 1V$$

$$V_G = 12 \times \frac{10}{30+10} = 3V$$

$$3 = V_{GSQ} + 0.5k I_{DSQ}$$

$$I_{DSQ} = 2m \times (V_{GSQ} - 1)^2$$

$$\Rightarrow (V_{GSQ}^2 - 2V_{GSQ} + 1) \times 2m \times 0.5k + V_{GSQ} = 3$$

$$\Rightarrow V_{GSQ}^2 - V_{GSQ} + 1 = 3$$

$$\Rightarrow (V_{GSQ} - 2)(V_{GSQ} + 1) = 0$$

$$V_{GSQ} = 2V$$

$$I_{DSQ} = 2m \times (2 - 1)^2 = 2mA$$

$$V_{DSQ} = 12 - 2m \times (2.5 + 0.5)k = 12 - 6 = 6V$$

