

Circuits and Electronics (I) Final Examination

Class: _____

ID: 102062129

Name: 許海輝

Choose all the correct answers in a question: (106%, you get 4 (or 5) points if your answer is correct, 0 point if you do not answer, but -1 (-2) point if your answer is incorrect)

- 3 1. The so-called 28nm process in IC fabrication means the [(1) channel length (2) channel width (3) oxide thickness (4) none of the above] of MOS is greater than 28nm, or equal to 28nm.

- 1,3 2. Which of the following breakdowns is a permanent failure in a MOS? [(1) PN-junction breakdown (2) Punch-through breakdown (3) Oxide breakdown (4) none of the above].

$$V_{th} \propto \frac{t_{ox}}{\epsilon_{ox}}$$

- 2 3. To [(1) decrease (2) increase (3) keep unchanged (4) none of the above] the V_{TN} of an enhancement nMOS, C_{ox} has to be decreased.

$$C_{ox} \propto \frac{\epsilon_{ox}}{t_{ox}} \downarrow$$

- 4 4. (5%) For an enhancement nMOS. Given $V_{TN}=0.8V$, $k_n=0.1mA/V^2$, $V_{GS} = 1.8V$, $V_A=50V$, $V_{DS} = 2$. What is the output resistance r_o of the circuit? [(1) 400k Ω (2) 200k Ω (3) 500k Ω (4) none of the above].

$$I_D = k_n (V_{GS} - V_{TN})^2$$

$$I_D = 0.1mA$$

$$k_n = \frac{1}{2} k_n' \frac{W}{L}$$

$$r_o = \frac{1}{I_D} \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{I_D} \frac{\partial}{\partial V_{DS}} [k_n (V_{GS} - V_{TN})^2]$$

- 2 5. (5%) For an enhancement pMOS. Given $k_p'=40\mu A/V^2$. Assume the drain current is 0.225mA when $V_{GS} = V_{DS} = -3V$ and the drain current is 1.4mA when $V_{GS} = V_{DS} = -4V$. What is the W/L ratio? (Hint: $V_{TP} < 0V$) [(1) 35.1 (2) 25.1 (3) 15.1 (4) 5.1].

$$V_{GS} < V_{GS} - V_{TN} \text{ at sat}$$

$$V_{TP} = -2.33$$

$$0.225mA = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$1.4mA = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\frac{0.225}{1.4} = \frac{(3 - V_{TN})^2}{(4 - V_{TN})^2}$$

$$\frac{225}{1400} = \frac{(3 - V_{TN})^2}{(4 - V_{TN})^2}$$

$$\frac{225}{1400} = \frac{9V_{TN}^2 + 6V_{TN} + 9}{V_{TN}^2 + 8V_{TN} + 16}$$

$$9V_{TN}^2 + 6V_{TN} + 9 = \frac{225}{1400} (V_{TN}^2 + 8V_{TN} + 16)$$

$$9V_{TN}^2 + 6V_{TN} + 9 = 0.1607V_{TN}^2 + 1.2856V_{TN} + 2.7312$$

$$8.8393V_{TN}^2 + 4.7144V_{TN} + 6.2688 = 0$$

$$V_{TN} = \frac{-4.7144 \pm \sqrt{4.7144^2 - 4 \cdot 8.8393 \cdot 6.2688}}{2 \cdot 8.8393}$$

$$V_{TN} = \frac{-4.7144 \pm \sqrt{22.224 - 222.224}}{17.6786}$$

$$V_{TN} = \frac{-4.7144 \pm \sqrt{-200}}{17.6786}$$

$$V_{TN} = \frac{-4.7144 \pm 14.142}{17.6786}$$

$$V_{TN} = \frac{-4.7144 + 14.142}{17.6786} = 0.534$$

$$V_{TN} = \frac{-4.7144 - 14.142}{17.6786} = -0.974$$

6. One way to make the threshold voltage of nMOS smaller is to [(1) decrease (2) increase (3) keep unchanged (4) none of the above] the impurity concentration of p-type substrate.

- 1, 2, 7. Which of the following statements about current in MOS circuit is correct? [(1) The MOS current will decrease when the temperature increases (2) The source, drain currents of a CMOS inverter circuit are 0 when the inverter is operated at non-switching, or stable state (3) The gate current in a normal MOS is always 0 (4) None of the above.]

- 1, 2, 4 8. Which of the following factors affects the value of threshold voltage of MOS? [(1) oxide thickness (2) oxide permittivity (3) channel length (4) substrate impurity concentration].

$$\downarrow \text{pMOS} \quad V_{TP} > 0$$

- 3 9. How about the variation of channel thickness (be distinguished from length, width) when negative V_{GS} is applied into the depletion mode pMOS? [(1) not changed (2) decrease (3) increase (4) depend on the relation of V_{GS} and V_{TP}].

- 4 10. (5%) Consider a depletion pMOS with $V_{TP}=2V$, $k_p=0.5mA/V^2$. What is the drain current when $V_{GS}=0V$, $V_{DS}=-1V$? [(1) 4mA (2) 3mA (3) 2.5mA (4) 1.5mA].

$$V_{DS} = -1 > V_{GS} - V_{TP} = -2 \quad \text{at triode}$$

$$I_D = 0.5m (2(-2)(-1) - 1)$$

$$= 0.5m \cdot 3$$

$$= 1.5m$$

- 1 11. The mechanism that the depletion region around the drain extends completely through the channel to the source terminal is called [(1) punch-through breakdown effect (2) body effect (3) Early effect (4) subthreshold conduction effect].

12. For a MOS circuit as shown in Fig. 1. Given $V_{TN}=2V$, $kn'=60\mu A/V^2$, and $W/L=60$.

- (a) (5%) What is the value of V_{GS} ? (1) 0.62V (2) 1.62V (3) 2.62V (4) 3.62V.
 (b) (5%) What is the value of drain current? (1) 1.76mA (2) 2.76mA (3) 3.76mA (4) 4.76mA.
 (c) (5%) What is the value of V_{DS} ? (1) 11.9V (2) 10.9V (3) 7.9V (4) 6.9V.

$$k = \frac{1}{2} \times 60 \times 60 = 1.8 \text{ mA}$$

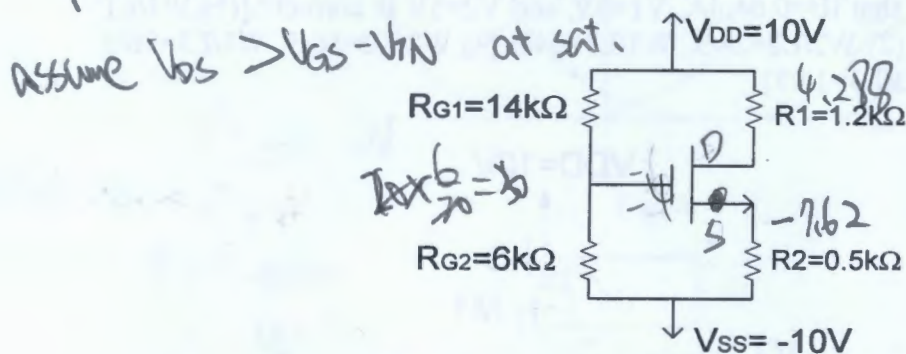


Fig. 1

$$V_{GS} = 10 - 0.5k I_D$$

$$= 10 - 0.5k I_D$$

$$I_D = \frac{(V_{GS} - 2)^2}{0.5k}$$

$$= 1.8 (V_{GS} - 2)^2$$

$$10 - V_{GS} = 0.9 (V_{GS}^2 - 4V_{GS} + 4)$$

$$0.9V_{GS}^2 - 2.6V_{GS} - 2.4 = 0$$

$$\frac{6.5}{1.8} \pm \frac{1.3}{1.8}$$

$$\frac{2.4 \pm \sqrt{2.6^2 + 0.9 \times 2.4 \times 4}}{1.8}$$

$$V_{GS} = 3.62 \text{ V}$$

13. Given an nMOS with $V_{TN0}=1V$, $\gamma=0.35V^{1/2}$, $\phi_f=0.4V$, what is the value of V_{TN} when $V_{SB}=2V$? [(1) 1.153V (2) 1.229V (3) 1.273V (4) none of the above].

$$1 + 0.35(\sqrt{0.8+2} - \sqrt{0.8})$$

14. What is the boundary equation of triode region and saturation region in nMOS?
 (1) $I_D = kn \times V_{DS}$ (2) $I_D = kn \times V_{GS}^2$ (3) $I_D = kn \times V_{DS}^2$ (4) $I_D = kn \times (V_{GS} - V_T)^2$


15. (5%) Given an nMOS with $V_{TN} = -1V$, $kn = 0.5 \text{ mA/V}^2$, $V_{DS} = 2V$, What is the value of I_{DSS} ? (1) 0mA (2) 2mA (3) 8mA (4) none of the above.

$$V_{GS} = 0$$

$$0.5 (1)^2$$

2 16. The effect that a change in V_{SB} alters the threshold voltage is called (1) punch-through breakdown effect (2) body effect (3) Early effect (4) subthreshold conduction effect.

4 17. (5%) Consider the circuit in Fig. 2. The transistor parameters are $V_{TN} = 1V$, $k_n' = 100 \mu A/V^2$ for all three transistors. Which width-to-length ratio required in each transistor such that $I_D = 0.64mA$, $V_1 = 3V$, and $V_2 = 5V$ is correct? (1) $W_1/L_1 = 4/5$, $W_2/L_2 = 16/5$ (2) $W_2/L_2 = 24/5$, $W_3/L_3 = 64/5$ (3) $W_2/L_2 = 16/5$, $W_3/L_3 = 96/5$ (4) $W_1/L_1 = 4/5$, $W_3/L_3 = 16/5$

 

M1 $V_{GS} = 5$
 $V_{DS} = 5 > V_{GS} - V_{TN} = 4$
 $0.64mA = 50 \mu \frac{W}{L} (4)^2$
 $\frac{W}{L} = \frac{4}{5}$

M2 $V_{GS} = 2$
 $V_{DS} = 2 > V_{GS} - V_{TN} = 1$
 $0.64 = 50 \mu \frac{W}{L} (1)^2$
 $\frac{W}{L} = \frac{50 \times 4}{5}$

M3 $V_{GS} = 3$
 $V_{DS} = 3$
 $0.64 = 50 \mu \frac{W}{L} (2)^2$
 $\frac{W}{L} = \frac{16}{5}$

Fig. 2

$AB + \overline{AB}$
 $(AB)'(A'B)'$

3 18. Given a CMOS logic circuit as shown in Fig. 3 where the pMOS network is not shown explicitly. What does the logic function Fig. 3 implement from V_o ? (1) $A+B'$ (2) $(A+B)'$ (3) $(A+B)(A'+B')$ (4) $(A'B + AB')$.

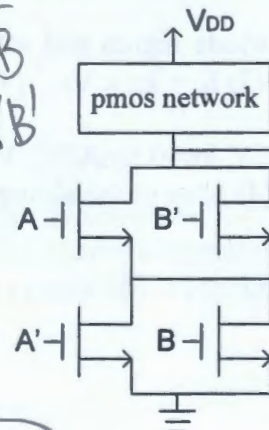


Fig. 3

$\overline{AB + A'B}$
 $(A+B')(A'+B)$
 $(A+B')' + (A'+B)'$
 $(A'B) + (AB')$


$AB + A'B'$

Truth Table:

A	B	V_o
0	0	1
0	1	1
1	0	0
1	1	0

 $\overline{(A+B')(A'+B)}$
 $(A+B) + (A'+B')$
 $A'B + AB$
 $(A'B) + (AB)$
 $A'B + AB$

 19. Which curve does a depletion pMOS probably behave in Fig. 4? (1)a (2)b (3)c (4)d.




$$V_{TP} > 0$$

$$V_{GS} < V_{TP}$$

Fig. 4

20. Consider the circuit in Fig. 5. The transistor parameters are $V_{TN1} = -2V$, $V_{TN2} = 1V$, $kn_1 = 10 \mu A/V^2$, $kn_2 = 80 \mu A/V^2$. If $V_I = 5V$,

 - (a) (5%)1 What is the value of V_O ? (1) 0.063V (2) 0.083V (3) 0.107V (4) 0.127V.
 (b) (5%)3 What is the value of I_{D1} ? (1) 80 μA (2) 60 μA (3) 40 μA (4) 0 μA .



M1 $V_{GS} = 0 > V_{TN1}$
 $V_{DS} > V_{GS} - V_{TN1} = 2$ at sat.

M2 $V_{GS} = 5$
 $V_{DS} < V_{GS} - V_{TN} = 4$ at triode

$$10 \mu [2]^2 = 80 \mu [(4) V_O - V_O^2]$$

$$1 = 2(4V_O - V_O^2)$$

$$V_O^2 - 8V_O + 1 = 0$$

$$\frac{8 \pm \sqrt{64 - 4}}{2}$$

$$4 \pm \frac{\sqrt{60}}{2}$$

$$3.873$$

- 4 21. Given a CMOS logic circuit as shown in Fig. 6 where the nMOS network is not shown explicitly. What is the Boolean function of V_o ? (1) $ABE + C' + D'$ (2) $A(BE + C' + D')$ (3) $(A'(B'E' + C + D))'$ (4) $A'B'E' + A'C + A'D$.

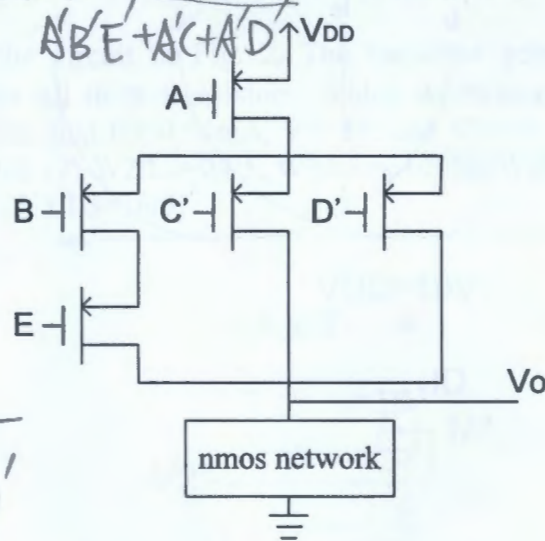


Fig. 6

$$ABE + AC' + AD'$$

$$(ABE') (AC')' (AD')$$

$$A(BE + C' + D')$$

$$A + (BE)(C')(D')$$

$$A'(BE') + AC' + AD'$$

$$ABC + AC' + AD'$$

$$(A+B+C)(A'+C)(A'+D)$$

$$A(B')$$

Have a Nice Summer Break !!

Thanks for your cooperation, looking forward to seeing you again in the future!