 



CS2102 Digital Logic Design
Exam 2 : 10:10 – 12:00, December 2, 2014

1. Consider the following circuit.



- Derive the Boolean expressions for T_1 through T_4 . (4%)
 - Write the outputs F_1 and F_2 as a function of the four inputs. (2%)
 - List the truth table with 16 combinations of the four input variables. Then list the binary values for T_1 through T_4 and outputs F_1 and F_2 in the table. (6%)
2. A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 3-input majority circuit by finding the circuit's truth table and a logic diagram. Your logic diagram must be a simplified two-level AND-OR circuit. (8%)
3. Let $F(A, B, C) = \Sigma(1, 2, 3, 6)$.
- Implement F using one 3-to-8 decoder and one OR gate. (4%)
 - Implement F using one 4-to-1 multiplexer. (4%)

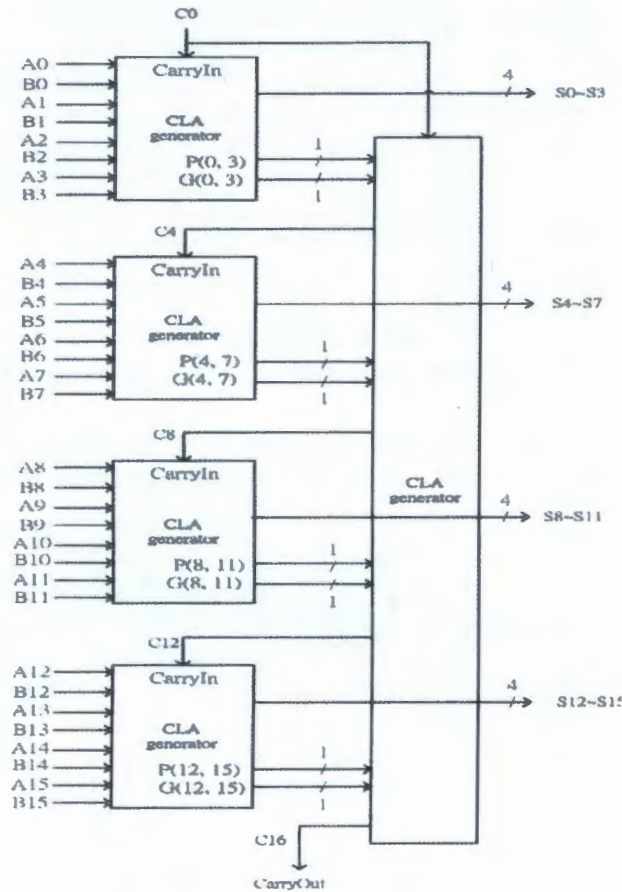
4. In class we have introduced a two-level carry lookahead (CLA) adder as shown below. The inputs of the adder include two 16-bit numbers $A = A_{15}A_{14}...A_0$ and $B = B_{15}B_{14}...B_0$, and a carry-in bit C_0 in the least significant position. In each significant position i ($0 \leq i \leq 15$), let S_i and C_{i+1} respectively denote the sum bit and carry-out bit of $A_i + B_i + C_i$. Explain how to get C_{12} , C_{15} , and S_{15} from this circuit. (12%)



pic
+9

 5. Consider the following sequential circuit that has two inputs x , y and one output sum . It consists of a full-adder and a D flip-flop, where C_{in} is the carry-in of the full-adder and C_{out} is the carry-out connected to the D flip-flop.

- Derive the input equations for the D flip-flop in terms of x , y , C_{in} . (2%)
- Derive the state equations for the D flip-flop in terms of x , y , C_{in} . (2%)
- Derive the state table of the sequential circuit. (6%)




(1 31)
1 2)

6. Consider the following state table

Present State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
a	f	b	0	0
b	d	a	0	0
c	f	b	0	0
d	g	a	1	0
e	d	e	0	0
f	f	b	1	1
g	g	d	0	1
h	g	a	1	0


$h = d$
 $e = b$
 $c = a$

 - (a) Is it a Moore or Mealy circuit? Why? (2%)
 (b) Perform state reduction to get the reduced state table. (4%)
 (c) Draw the state diagram corresponding to the reduced state table. (4%)
7. Use D flip-flops and other necessary gates to design a sequential circuit whose state diagram is shown below. You need to simplify the input equation of each D flip-flop using the K-map method to build your circuit (10%)




$JQ' + K'Q$

 8. (a) Complete the following timing diagram for a negative-edge-triggered J-K flip-flop. Assume Q begins at 1, and ignore the propagation delay of the J-K flip-flop. (4%)



 - (b) Complete the following timing diagram for a positive-edge-triggered T flip-flop with an asynchronous active-low reset input. Assume Q begins at 1, and ignore the propagation delay of the T flip-flop. (6%)



9. Answer TRUE or FALSE. (6%)

- (a) A Verilog module can be defined within another Verilog module.
- (b) The instance name of a Verilog module is required.
- (c) The first entry in the port list of a Verilog predefined primitive is an input.

10. Use each of the following styles to complete a Verilog model that describes one-bit comparator whose output is 1 if in_1 is greater than or equal to in_2, where in_1, in_2 are the inputs, and comp_out is the output. Assume that each input has the value 0 or 1. (9%)

(a) Gate-level modeling

```
module test_a (comp_out, in_1, in_2);
    output comp_out;
    input in_1, in_2;
    /* complete your code here */
endmodule
```

(b) Dataflow modeling

```
module test_b (comp_out, in_1, in_2);
    output comp_out;
    input in_1, in_2;
    /* complete your code here */
endmodule
```

(c) Behavioral modeling

```
module test_c (comp_out, in_1, in_2);
    output comp_out;
    input in_1, in_2;
    /* complete your code here */
endmodule
```

11. Explain why the following Verilog module does not correctly model a 4-to-1 multiplexer. (5%)

```
module mux4 (a, b, c, d, select, y_out);
    input a, b, c, d;
    input [1:0] select;
    output y_out;

    reg y_out;

    always @ (select)
        if (select == 0) y_out = a;
        else if (select == 1) y_out = b;
        else if (select == 2) y_out = c;
        else y_out = d;
endmodule
```

01

(b) $F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D$
 $F_2 = T_2 + D' = A'B + D'$

(c)


A	B	C	D	T ₁	T ₂	T ₃	T ₄	F ₁	F ₂
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1	0
0	0	1	0	1	0	1	0	1	1
0	0	1	1	1	0	1	1	1	0
0	1	0	0	0	1	0	1	1	1
0	1	0	1	0	1	0	0	0	1
0	1	1	0	0	1	0	1	1	1
0	1	1	1	0	1	0	0	0	1
1	0	0	0	0	0	1	0	1	1
1	0	0	1	0	0	1	1	1	0
1	0	1	0	1	0	1	0	1	1
1	0	1	1	1	0	1	1	1	0
1	1	0	0	0	0	1	0	1	1
1	1	0	1	0	0	1	1	1	0
1	1	1	0	0	0	1	0	1	1
1	1	1	1	0	0	1	1	1	0

2.


x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

x \ yz	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$F = xz + yz + xy$

 


3, (a)

 

(b)

A	B	C	T
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

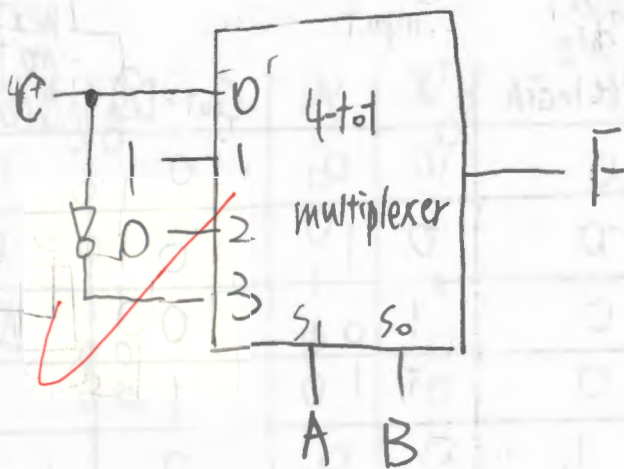

4,

Let $p_i = A_i \oplus B_i$
 $g_i = A_i \cdot B_i$

$$C_{12} = P_{(8,11)} C_8 + G_{(8,11)} = P_{(8,11)} (P_{(4,7)} C_4 + G_{(4,7)}) + G_{(8,11)}$$

$$= P_{(8,11)} G_{(4,7)} + G_{(8,11)} + P_{(8,11)} P_{(4,7)} (P_{(0,3)} C_0 + G_{(0,3)})$$

$$= P_{(8,11)} P_{(4,7)} P_{(0,3)} C_0 + P_{(8,11)} P_{(4,7)} G_{(0,3)} + P_{(8,11)} G_{(4,7)} + G_{(8,11)}$$

$$C_{15} = p_{14} C_{14} + g_{14} = p_{14} (p_{13} C_{13} + g_{13}) + g_{15} = p_{14} p_{13} (p_{12} C_{12} + g_{12}) + p_{14} g_{13} + g_{14}$$

$$= p_{14} p_{13} p_{12} C_{12} + p_{14} p_{13} g_{12} + p_{14} g_{13} + g_{14}$$

$$S_{15} = A_{15} \oplus B_{15} \oplus C_{15}$$

5. (a)

$$D = xy + x\bar{c}in + y\bar{c}in = xy + xQ(t) + yQ(t)$$


(b)

$$Q(t+1) = D = xy + x\bar{c}in + y\bar{c}in = xy + xQ(t) + yQ(t)$$

(c)

Present state $Q(t) = \bar{c}in$	Input $X \quad Y$		Count = D	next state $Q(t+1)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1


Sum = 2

6. (a) Mealy,  edge-triggered 發生前的情況判斷 output

(b)

Present state	Next state		Output	
	$X=0$	$X=1$	$X=0$	$X=1$
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

(c)

 

7.

Present state

A B
00
00
01
01
10
10
11
11

Input

X
0
1
0
1
0
1
1

Next state

A B
00
01
01
11
00
00
11
10

D_A

0
0
0
1
0
0
1
1

D_B


0
1
1
1
0
0
0
0

D _A	A	B	X
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1

$$D_A = BX + ABX'$$

D _B	A	B	X
0	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1

$$D_B = AB + A'X + BX'$$

 

8. -0

9. (a) False
 (b) True
 (c) False

10.

(a) wire in_2_not, equal, greater;

not G1(in_2_not, in_2);

and G2(greater, in_1, in_2_not);

xor G3(equal, in_1, in_2);

- 3

or G4(comp_out, greater, equal);

(b) assign comp_out = (in_1 > in_2) || (in_1 == in_2);

✓

(c)

always @ (in_1, in_2) begin

if (in_1 > in_2)

comp_out = 1'b1;

if (in_1 == in_2)

comp_out = 1'b1;

if (in_1 < in_2)

comp_out = 1'b0;

end

- 1

11. 沒有 else if 應改成

- always @ (select)

```
if (select == 2'b00) y-out = a;
```

```
if (select == 2'b01) y-out = b;
```

```
if (select == 2'b10) y-out = c;
```

```
if (select == 2'b11) y-out = d;
```