

CS2102 01 Digital Logic Design Midterm 1 (10:10am-12:00pm, Oct 28th)

Truth or False (24%):

(Write down T or F. You don't need to give the reason.)

1. _____ According to the duality principle, $x + 1 = 1$ and $x \cdot 1 = x$ are dual functions.
2. _____ The addition of a positive number and a negative number, both in 2's complement form, will not produce an overflow.
3. _____ The n -bit signed-2's complement system can represent 2^n different integers, ranging from -2^{n-1} to $2^{n-1} - 1$.
4. _____ Any Boolean function can be represented by either of the 2 unique canonical forms, namely, sum-of-products or product-of-sums forms.
5. _____ The AOI implementation represents the AND-OR-INVERT implementation, which can be obtained by the complement of sum-of-products form.
6. _____ Each K-map defines a unique Boolean function.
7. _____ It is possible that nonstandard forms can have fewer literals than standard forms.
8. _____ AND gate is a universal gate because any Boolean function can be implemented by AND gates only.

Answer the following questions: (76%)

(Write down your intermediate results. Do not give the final answer only.)

1. (11%) [Conversion] Number conversions:
 - (a) (4%) Convert the $(452.4)_8$ to hexadecimal.
 - (b) (4%) Convert $(32.0625)_{10}$ to octal number.
 - (c) (3%) Represent -73 in the 8-bit signed-magnitude representation.
2. (6%) [2's Complement] Show the detailed procedure of the following additions with 7-bit binary numbers, using 2's complement for negative numbers. You should also translate the result to decimal, and indicate if there is an overflow.
 - (a) (3%) $(-15) + (-50)$;
 - (b) (3%) $(+28) - (+49)$.
3. (5%) [Canonical] Use the brief notation \sum or Π to express the Boolean function $F(a, b, c, d) = (ad + b'c + bd')(b + d)$ in **product-of-maxterms**.
4. (5%) [Multi-level] Draw the multi-level NAND circuit for $F = w(x + z') + xz'$ by using NAND gates only. You don't need to simplify the Boolean function. Assume that both the normal and complement inputs are available.
5. (13%) [K-Map] For the Boolean function $F(w, x, y, z) = xy'z + x'y'z + w'xy + wx'y + wxy$,
 - (a) (5%) Use K-map to simplify F to **sum-of-products form**;
 - (b) (5%) Draw the two-level AND-OR logic diagram of F . Assume that both the normal and complement inputs are available.
 - (c) (3%) Draw the OAI implementation of F . Assume that both the normal and complement inputs are available.
6. (10%) [EPI] Consider the Boolean function $F(A, B, C, D) = \Pi(3, 4, 6, 11, 12, 14)$.

- (a) (5%) List all the prime implicants (PIs) and essential prime implicants (EPIs).
- (b) (5%) List all the possible simplified functions of F in **sum-of-products** form.
7. (10%) [**Don't-Care**] Simplify the Boolean function $F(A, B, C, D) = \sum(1, 5, 9, 11, 15)$ with the don't-care condition $d(A, B, C, D) = \sum(0, 3, 6, 8, 13)$ in **product-of-sums** form. And then implement the simplified function with a two-level NOR circuit. Assume that both the normal and complement inputs are available.
8. (6%) [**Boolean Algebra**] Prove the validity of Theorem 6(b): $x(x + y) = x$ by using Boolean algebra.

Table 2.1*Postulates and Theorems of Boolean Algebra*

| | | | | |
|---------------------------|-----|-----------------------------|-----|---------------------------|
| Postulate 2 | (a) | $x + 0 = x$ | (b) | $x \cdot 1 = x$ |
| Postulate 5 | (a) | $x + x' = 1$ | (b) | $x \cdot x' = 0$ |
| Theorem 1 | (a) | $x + x = x$ | (b) | $x \cdot x = x$ |
| Theorem 2 | (a) | $x + 1 = 1$ | (b) | $x \cdot 0 = 0$ |
| Theorem 3, involution | | $(x')' = x$ | | |
| Postulate 3, commutative | (a) | $x + y = y + x$ | (b) | $xy = yx$ |
| Theorem 4, associative | (a) | $x + (y + z) = (x + y) + z$ | (b) | $x(yz) = (xy)z$ |
| Postulate 4, distributive | (a) | $x(y + z) = xy + xz$ | (b) | $x + yz = (x + y)(x + z)$ |
| Theorem 5, DeMorgan | (a) | $(x + y)' = x'y'$ | (b) | $(xy)' = x' + y'$ |
| Theorem 6, absorption | (a) | $x + xy = x$ | (b) | $x(x + y) = x$ |

Show your proof by using postulates and theorems other than Theorem 6(a)(b) in the table. You should identify specific postulate or theorem to justify each step (**do not** use Theorem 6(a)(b)). Do not use the truth table.

9. (10%) [**Design**] Design a voting machine F for four people, say, A , B , C and D . Each person sets his/her input as 1 when he/she agrees with some certain topic to be voted. Otherwise, he/she votes for 0 if he/she disagrees. The output of the machine will be 1 if three (75%) or four (100%) persons agree with the topic.
- (a) (4%) List the truth table of the voting machine F .
- (b) (3%) Use K-map to derive the simplified **sum-of-products** function.
- (c) (3%) Draw the corresponding NAND-NAND logic diagram. Assume that both the normal and complement inputs are available.

Good luck and happy examination!!

If you have too much time left, there is a joke for you:

A professor was giving a big test one day to his students. Once the test was over the students all handed the tests back in. The professor noticed that one of the students had attached a \$1000 bill to his test with a note saying "Ten dollars per point."

The next class the professor handed the tests back out. This student got back his test, an envelope with \$620 change, and a note saying "Thanks..."