 


**(Note: inverted inputs are allowed)**

1. (12%) Find a minimum (shared) two-level, multiple-output NOR-NOR circuit to realize  $f_1(A, B, C, D) = \sum m(0, 2, 4, 6, 7, 10, 14)$  and  $f_2(A, B, C, D) = \prod M(2, 3, 6, 8, 9, 11, 12, 13, 15)$ . (Note:  $m_7 = A'BCD$ ,  $M_7 = (A + B' + C' + D')$ ).

Ans:



2. (6%) Complete the timing diagram for the circuit as shown in Fig. 1 (Y from 1~28ns, Z from 3~28ns). Assume the AND gate has delay of 1ns and the NOR gate has delay of 3ns.



 


Fig. 1

 

Ans:

 


3. (13%) Consider the function  $F(A, B, C, D) = \sum m(0, 2, 5, 6, 7, 8, 9, 12, 13, 15)$ . (a) (3%) Find a minimum AND-OR circuit which implements F. (b) (6%) Identify two 1-hazards in your implementation. (c) (4%) Find an AND-OR circuit for F which has no hazards.

Ans:

 
8.10 (a)  $F(A, B, C, D) = \sum m(0, 2, 5, 6, 7, 8, 9, 12, 13, 15)$

There are 3 different minimum AND-OR solutions to this problem. The problem asks for any two of these.




$$F = BD + AC' + A'C'D' + B'C'D'$$

 Solution 1: 1-hazards are between  
0000 ↔ 0010 and 0111 ↔ 0110



$$F = BD + AC' + A'B'D' + A'BC$$

 Solution 2: 1-hazards are between  
0010 ↔ 0110 and 0000 ↔ 1000



$$F = BD + AC' + A'B'D' + A'C'D'$$

Solution 3: 1-hazards are between  
0111 ↔ 0110 and 0000 ↔ 1000  
Without hazards:

$$F' = BD + AC' + B'C'D' + A'CD' + A'B'D' + A'BC$$

8.10 (b)

4. (4%) Explain these two terms. (a) (2%) Verification. (b) (2%) Testing.

Ans: Omitted

5. (12%) Given a logic circuit as shown in Fig. 2. According to the SPEC, with applying the input vector  $(A, B, C, D) = (1, 1, 0, 0)$ , the output value at W should be 0. However, the actual simulation result is 1. Assume the possible errors are only either AND ↔ OR, or Inverter ↔ Buffer, and only one error occurs at a time. Please indicate three possible error locations in which a single error occurs.

 


Fig. 2

Ans: G6, or G4, or G3

6. (6%) Implement the function  $G(A, B, C) = \sum m(0, 4, 6, 7)$  using a 4-to-1 MUX with selection inputs A and B as shown in Fig. 3. (Note:  $m_3 = ABC = 011$ , and when  $AB=10$ ,  $I_2$  will be selected). (Hint: To determine the  $I_0 \sim I_3$ .)


 


Fig. 3

Ans:  $I_0 \sim I_3 = c', 0, c', 1$

7. (5%) Implement the function  $G = A'B' + AB$  using two three-state (tri-state) buffers and one inverter. Assume  $B$  is the control line of three-state buffers.

Ans:

 

8. (6%) Given  $F = ABC + DE' + A'BE + BD'E$ . Expand  $F$  about the variables  $A$  and  $B$ .

Ans:  $A'B'(DE') + A'B(DE' + E) + AB'(DE') + AB(C + DE' + D'E)$

9. (12%) The PLA in Fig. 4 will be used to implement for the following equations:

$$X = ABD + A'C + BC + CD$$

$$Y = A'C + AC' + C'D'$$

$$Z = CD + A'C + ABD$$

Indicate the connections that will be made to program the PLA to implement these equations.


 


Fig. 4

Ans:

 


10. (6%) Given a falling-edge-trigger U-V Flip-Flop whose truth table is as shown in Fig. 5. Please implement this U-V Flip-Flop by using a falling-edge-trigger S-R Flip-Flop and other logic gates if necessary.

U	V	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	Inputs are not allowed
1	0	1	Inputs are not allowed
1	1	0	1
1	1	1	1

Fig. 5

Ans:

 

11. (8%) Given a sequential circuit consists of four T Flip-Flops as shown in Fig. 6. Assume the initial state  $Q_4Q_3Q_2Q_1$  is 0000. Draw the state graph of this circuit. (That is, the state sequence from the initial state 0000).

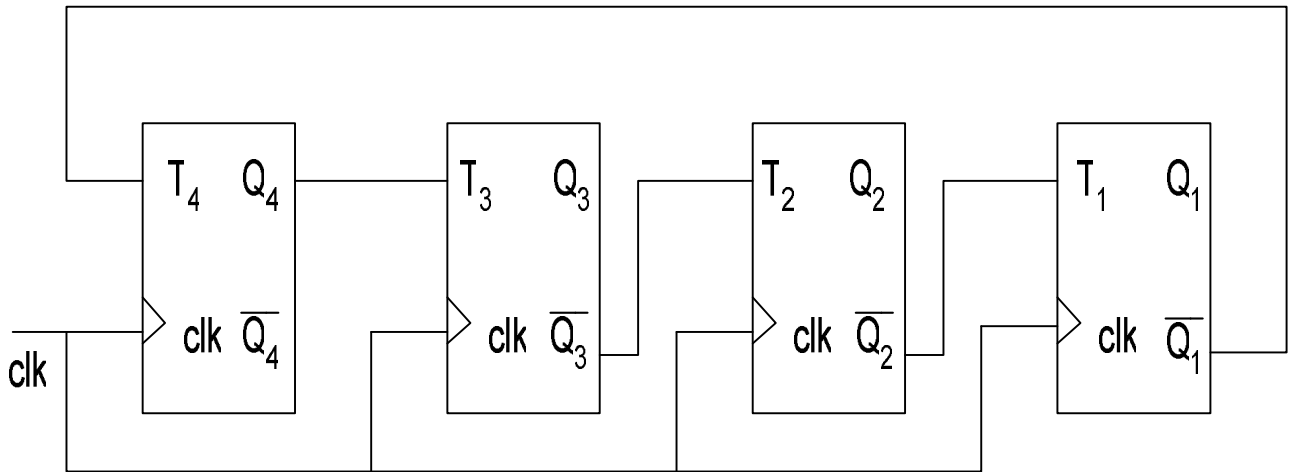


Fig. 6

Ans: 0000  $\rightarrow$  1011  $\rightarrow$  1101  $\rightarrow$  1000  $\rightarrow$  0111

12. (10%) Design a 4-bit bi-directional rising-edge-trigger shift register as shown in Fig. 7. Inputs are (clk,  $D_4 \sim D_1$ , SIL, SIR, SHL, SHR); output are ( $Q_4$ ,  $Q_1$ ). Its operations are summarized in the following table. (Hint: you may need four D Flip-Flops and 4 MUXes for the design.)


 


Fig. 7

SHL	SHR	Operations
0	0	Data remain intact
0	1	Shift right, the leftmost FF get the data from SIL and the rightmost FF shift out the date at Q <sub>1</sub>
1	0	Shift left, the rightmost FF get the data from SIR and the leftmost FF shift out the date at Q <sub>4</sub>
1	1	Load D <sub>4</sub> ~D <sub>1</sub> to the register

Ans:

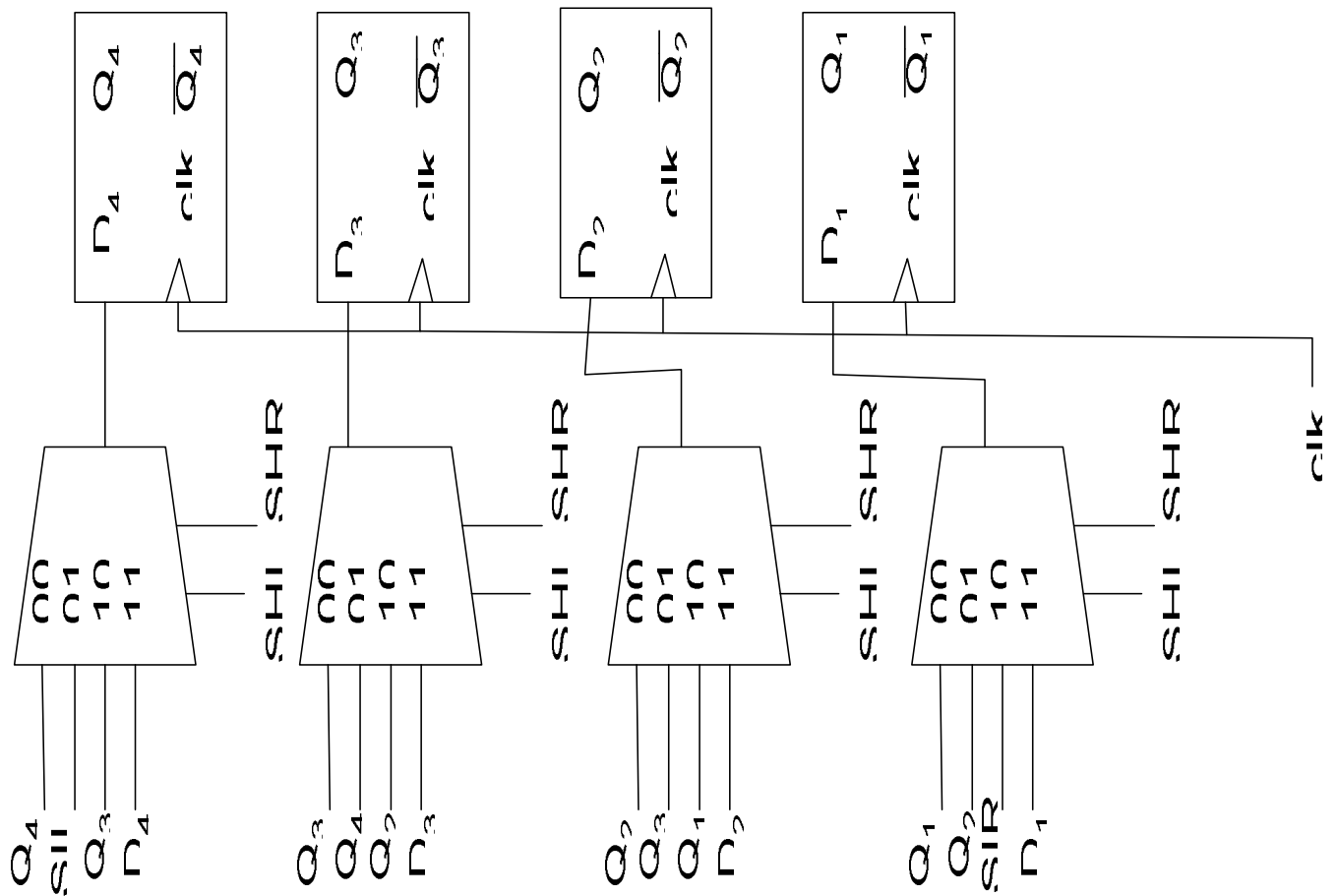



13. (6%) Bonus: What are three wishes made by the man, the woman, and the guy from Magic Lamp in the joke I talked during the course?

Ans: Omitted