


# CS2102 Second Midterm Exam

10:10-11:50am, Thursday, November 26, 2009

Department of Computer Science  
National Tsing Hua University

Note: Maximal Score = 110分

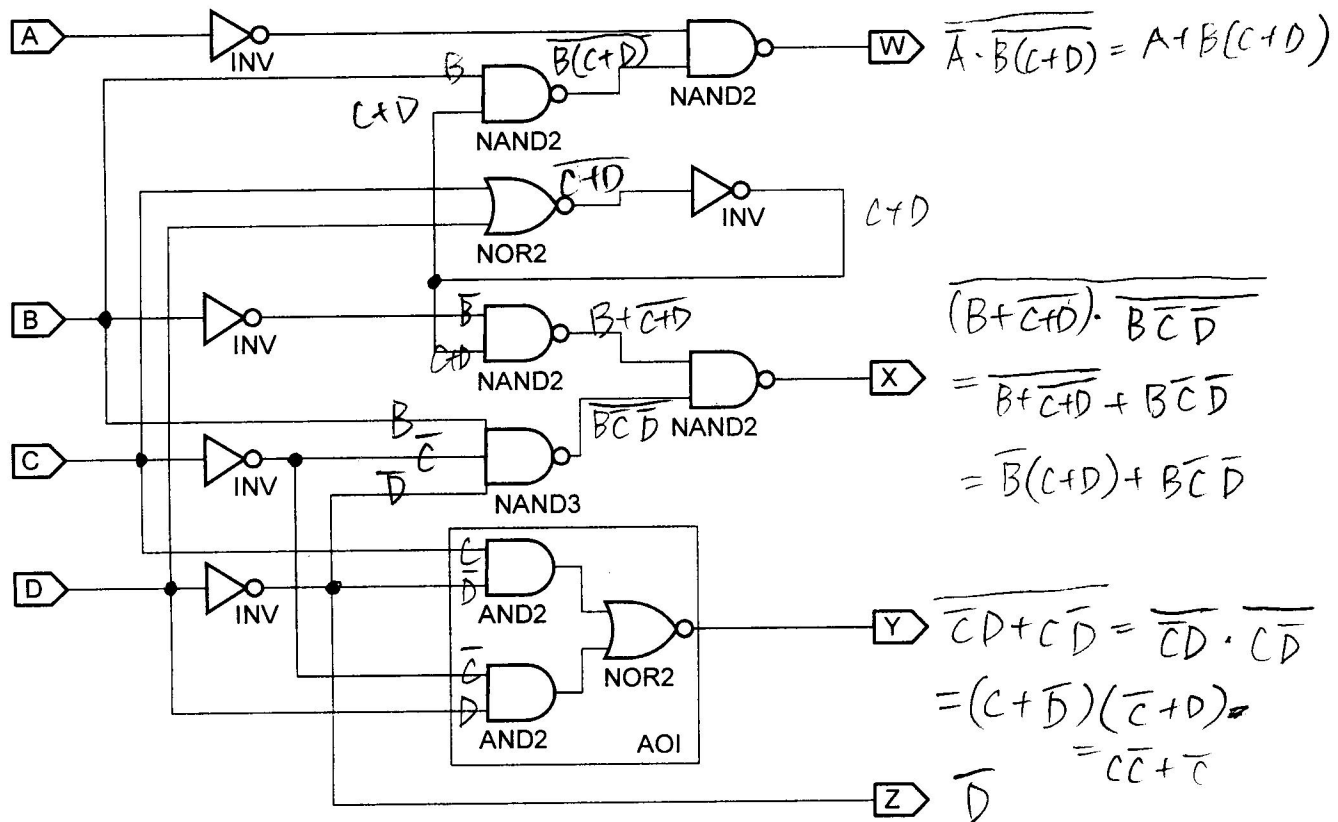1. (15pts) Derive a truth table for the following circuit. What is its function?



2. (15 pts) Given two 4-to-2 priority encoders. Design a 8-to-3 priority encoder by adding to them some circuits. Name the encoder's valid flag V, outputs  $X_2, X_1, X_0$  and inputs  $A_7, A_6, \dots, A_0$  with  $A_7$  having the highest priority. For example, when  $A = 0010\ 0110$ , X should equals 101 and  $V = 1$ , while when  $A = 0000\ 0000$ , V should equals 0.

(3) (10 pts) Represent  $-149.375_{10}$  in 14-bit (9 bits before and 5 bits after radix point)

- A. Signed-magnitude Binary format
- B. One's Complement Binary Format
- C. Two's Complement Binary Format

Handwritten conversion of  $-149.375_{10}$  to binary:

Integer part:  $149_{10} \rightarrow 10010101_{2}$

Fractional part:  $0.375_{10} \rightarrow 0.011_{2}$


Final 14-bit representation:  $10010101.011$

- 10 4. (10pts) Given a 8-to-1 multiplexer. Design a 4-input-1-output combinational function that output 1 when the input has equal number of 1s and 0s, and output 0 otherwise.

1 | 0


- 10 5. (20 pts) Analyze the following circuit:

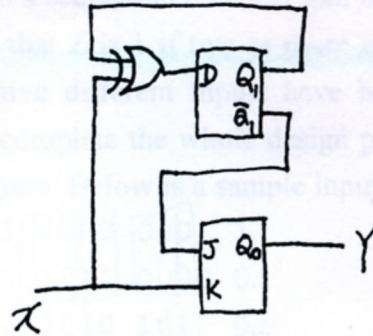- Derive the state table
- Derive the state transition diagram
- Simplify your diagram by merging equivalent states if possible.



Y	0	1	1	1	0	1	1	1	0	0	0
X	1	0	0	0	1	0	0	0	0	1	0

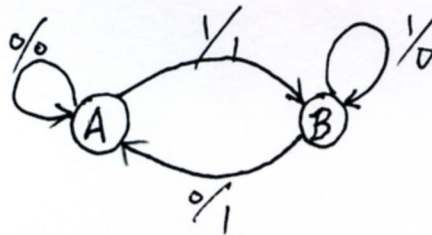6. (15 pts) Design a circuit implementing the following state transition diagram. Use one positive edge-triggered D-type flip-flop.



- 25 7. (10 pts) Given a D-type flip-flop. Add some circuit to it to make a JK flip-flop.

8. (15 pts) Design a string recognizer with input X and output Y for the pattern 11011. For example,

30

X = 1001 1011 0110 1111 0110 0...

Y = 0000 0001 0010 0100 0010 0...

Just draw a **Mealy** style state transition diagram. Note that a Mealy machine's output depends on both state and input.

9. (15 pts) Design a sequential machine that has two binary inputs X and Y, and one output Z such that Z is 1 if two or more consecutive identical inputs, or two or more consecutive different inputs have been observed, and 0 otherwise. You don't have to complete the whole design process. Just draw a **Moore** style state transition diagram. Below is a sample input and output sequences of the machine.

X = 0111 1000 0001 1...  
 Y = 1100 1011 0000 0...  
 Z = 0000 1010 1011 0...