

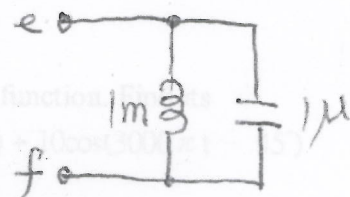
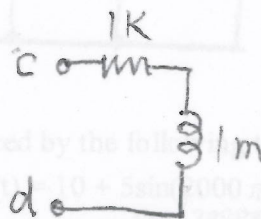


**NOTE:** 每一題都要寫出計算過程


- (20%) For a sinusoidal signal  $v(t) = 10\cos(100\pi t + 45^\circ)$ 
  - What is its peak value?  $10$
  - What is its root-mean-square value?  $5\sqrt{2}$
  - What is its frequency?  $50$
  - What is its angular frequency?  $100\pi$
  - Express it in phasor form.
  - How much power is consumed if it is applied to a  $10\Omega$  resistor?
  - How much power is consumed if it is applied to a  $1\mu\text{F}$  capacitor?  $0$   
 $10^{-6}$
- (15%) Find equivalent impedance  $Z_{ab}$ ,  $Z_{cd}$ , and  $Z_{ef}$  when the working frequency  $f = 1000/2\pi \text{ Hz}$ .

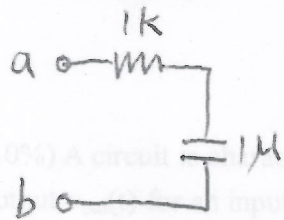

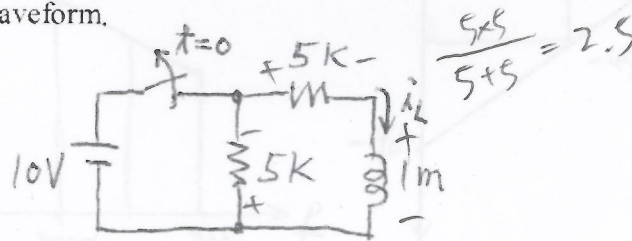- (15%) For the circuit below,
  - What is  $i_L(t^+)$ ?
  - Draw its waveform.




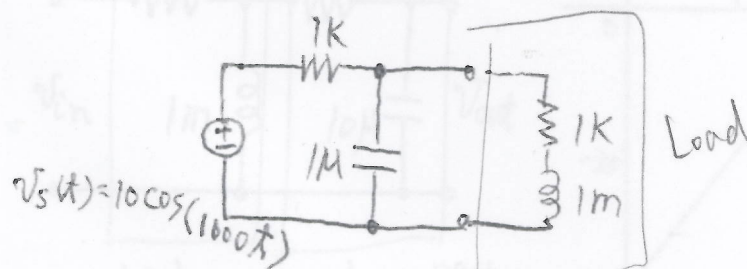- (15%) Treat the circuit below as cascade of two filters. Determine the values of
  - Find the Thevenin equivalent circuit
  - Calculate power delivered to the load (combination of R and L).
  - What is the power factor?




$$\frac{1050 - 49j}{\sqrt{1104910}} = 1051$$

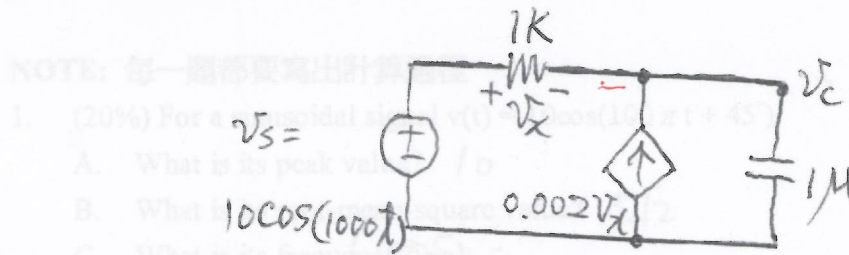
5. (10%) Find steady-state  $v_C(t)$  of the following circuit.



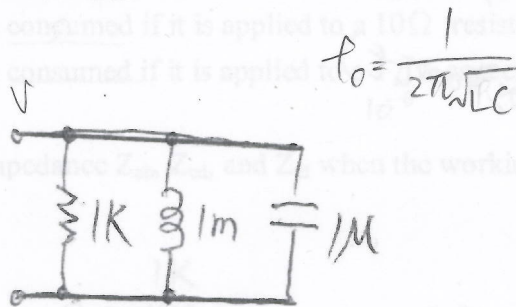6. (10%) Find the resonant frequency of the circuit below.



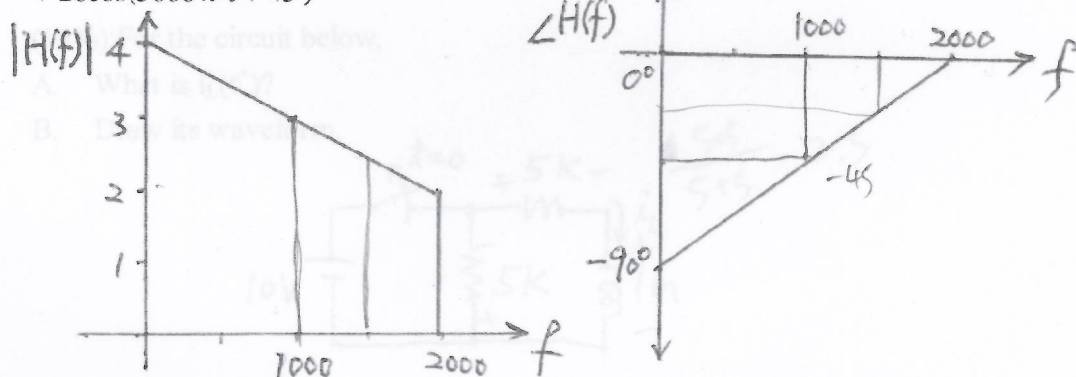7. (10%) A circuit is characterized by the following transfer function. Find its output  $v_{out}(t)$  for an input  $v_{in}(t) = 10 + 5\sin(2000\pi t + 30^\circ) + 10\cos(3000\pi t - 45^\circ) + 20\cos(5000\pi t + 45^\circ)$



8. (15%) Treat the circuit below as cascade of two filters. Determine the values of  $R_1$  and  $R_2$  such that the transfer function as shown in the Bode Plot is obtained.

