

= F

2015 Spring CS210001 Circuits and Electronics (I) Midterm II

Class: _____

ID: 102062129

Name: 許敬軒

Part One: Calculation (78%)

1. (29%) For the voltage regulator circuit in Fig. 1, let $V_Z = 5.6\text{V}$ at $I_{ZT} = 2\text{mA}$, $r_Z = 50\Omega$, $R = 0.5\text{k}\Omega$, $I_{ZK} = 0.2\text{mA}$.
 - (a) (7%) Show that $V_O = (R/(R+r_Z)) V_{Z0} + (r_Z/(R+r_Z)) V_S - (R/r_Z) I_L$, if Zener diode is operated in the breakdown region.
 - (b) (3%) If $V_S = 10\text{V}$, $R_L = \infty$, determine V_O .
 - (c) (4%) If $V_S = 10 \pm 1\text{V}$ ($\Delta V_S = \pm 1\text{V}$), $R_L = \infty$, determine ΔV_O and line regulation as compared with (b).
 - (d) (6%) If $V_S = 10\text{V}$, $R_L = 4\text{k}\Omega$, determine ΔI_L and load regulation as compared with (b). The load regulation is a negative value, what is the meaning of this sign?
 - (e) (3%) If $V_S = 10\text{V}$, $R_L = 0.5\text{k}\Omega$, determine V_O .
 - (f) (6%) If $V_S = 10 \pm 1\text{V}$, determine the minimum R_L such that the Zener diode is operated in the breakdown region.

$$I_{\min} = 0.2\text{mA}$$

$$r_Z = 50\Omega$$

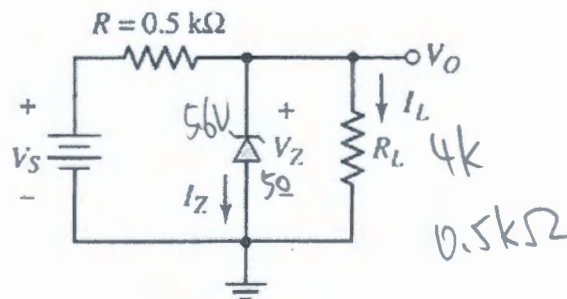


Fig. 1

2. (8%) Design a clipping circuit such that its input and output waveforms are as shown in Figs. 2(a) and 2(b), respectively. Assume the $V_r = 0.7$ V. Remember to indicate the V_o terminals in your design.

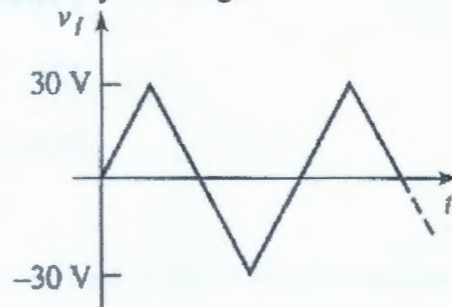


Fig. 2(a)

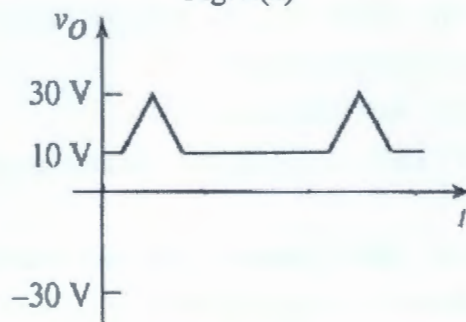


Fig. 2(b)

3. (6%) Consider the circuit in Fig. 3. The cut-in voltage of each diode is $V_r = 0.7$ V.
 (a) For $R = 2.5 \text{ k}\Omega$, determine I_{D1} , I_{D2} and V_A . (b) Find R such that $V_A = 0$, what are the values of I_{D1} and I_{D2} .

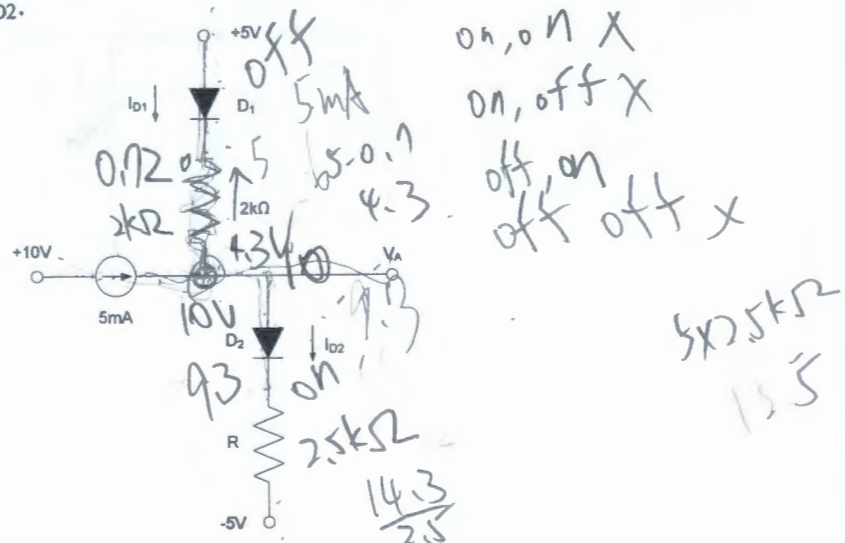


Fig. 3

4. (4%) Determine the Boolean expression for V_O in terms of the five input voltages for the circuit in Fig. 4.

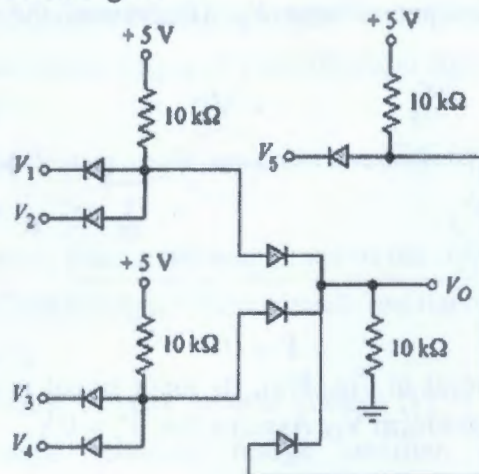


Fig. 4

5. (6%) Let $V_r = 0.7\text{ V}$ for the diode in the circuit of Fig. 5. Determine I_D and V_D when $V_1 = 12\text{ V}$, $V_2 = 16\text{ V}$.

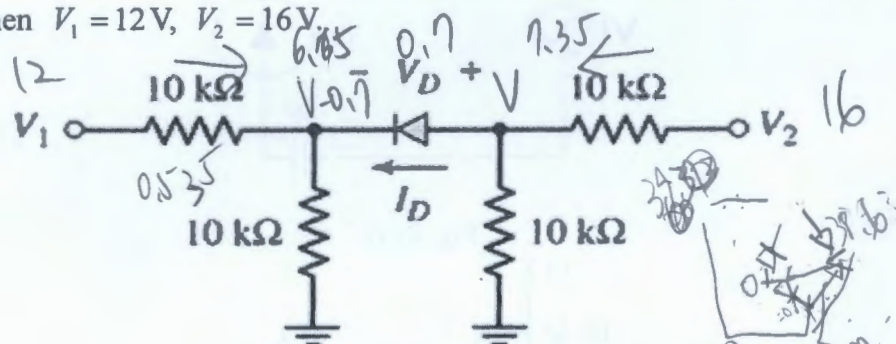


Fig. 5

6. (5%) Consider the circuit in Fig. 6(a), its input signal is as shown in Fig. 6(b). Drawing the output waveform V_O . (Label all the appropriate values in the waveform.)

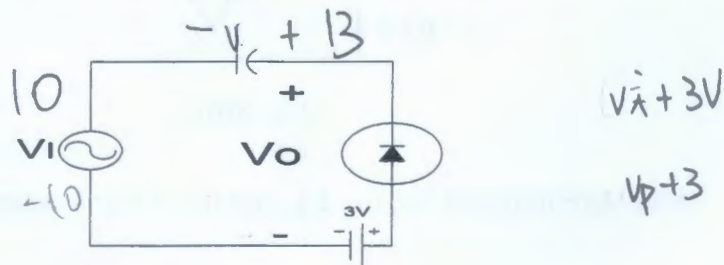


Fig. 6(a)

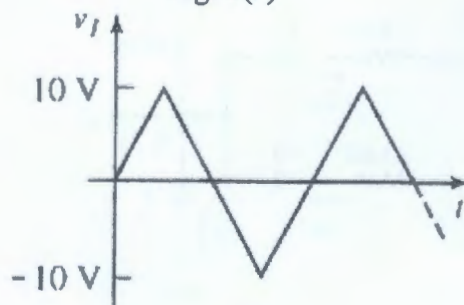


Fig. 6(b)

7. (6%) Consider the circuit in Fig. 7, $V_S = 10V$, $V_i = 0.1\sin(\omega t)V$, $R = 100\Omega$, $V_T = 26mV$, the diode has piecewise linear parameters of $n=2$, $V_r = 0.6V$ and $r_f = 30\Omega$. Calculate the output voltage V_O . (Expressed the V_O with DC and AC components.)

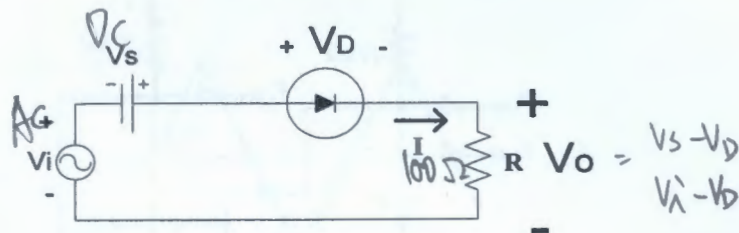


Fig. 7

8. (6%) Consider the circuit in Fig. 8(a), its input signal is as shown in Fig. 8(b). Drawing the output waveform V_O . Assume the $V_r = 0V$.

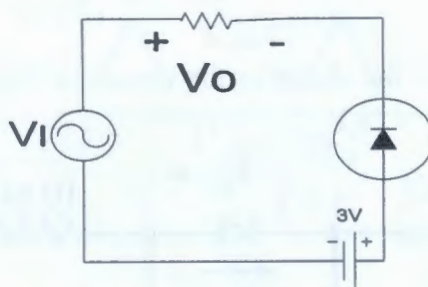


Fig. 8(a)

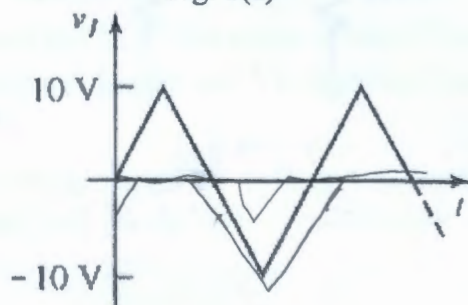


Fig. 8(b)

$$\begin{aligned} V_i &= 0 & V_O &= -3 \\ V_i < 0 & & V_O &= -3 + V_i \\ V_i \geq 3 & & V_O &= 0 \end{aligned}$$

9. (8%) Determine the V_O , I_{D1} , I_{D2} , and I_{D3} in Fig. 9 when $V_1 = 6V$, $V_2 = 2V$.

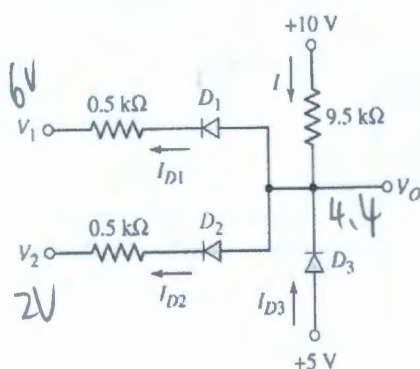


Fig. 9

Part Two: Brief Answer (22%)

1. (6%) List three applications of diode circuits that contain capacitors.
2. (3%) What are three major stages of a rectification circuit, i.e., input signal is AC, output signal is DC ?
3. (4%) What does the "cut-in angle" mean in a rectifier ? You can explain it using a figure.
4. (4%) State two ways to reduce the magnitude of the ripple voltage.
5. (2%) What is the small-signal incremental resistance r_d of a diode? Use an equation to express it.
6. (3%) What is the value of peak inverse voltage (PIV) of diodes in center-tapped transformer full-wave rectifier, bridge rectifier, and half-wave rectifier, respectively? Assume that the input signal is $V_p \sin(\omega t)V$ and the cut-in voltage of the diode is V_r .

波形

1.

$$(a) \quad I = \frac{V_s - V_o}{R}$$

$$I_z = I - I_L$$

$$V_o = V_{z0} + r_z \cdot I_z$$

$$V_o = V_{z0} + r_z \left[\frac{V_s - V_o}{R} - I_L \right]$$

$$V_o = V_{z0} + \frac{r_z}{R} \cdot V_s - \frac{r_z}{R} V_o - r_z I_L$$

$$\left(1 + \frac{r_z}{R}\right) V_o = V_{z0} + \frac{r_z}{R} V_s - r_z I_L$$

$$V_o = \frac{R}{R+r_z} V_{z0} + \frac{r_z}{R+r_z} V_s - (R/r_z) I_L \quad \#$$

(b)

$$5.6 = V_{z0} + 2m \cdot 50$$

$$V_{z0} = 5.6 - 0.1 = 5.5 \text{ V}$$

$$I = \frac{10 - 5.5}{0.5k + 50} = \frac{4.5}{550} = 8.18 \times 10^{-3}$$

$$5.5 + \frac{9}{1100} \times 50 = 5.909$$

$$A: V_o = 5.909 \text{ V} \quad \checkmark$$

(c)

$$\left. \frac{\Delta V_o}{\Delta V_s} \right|_{\Delta I_L=0} = \frac{r_z}{R+r_z} = \frac{50}{550} = \frac{1}{11} \quad \checkmark$$

$$\Delta V_o = \frac{1}{11} \times 2 = \frac{2}{11} \quad \checkmark$$

$$A: \Delta V_o = \frac{2}{11} \text{ V}$$

$$\text{line regulation} = \frac{1}{11}$$

(d) $\left. \frac{\Delta V_o}{\Delta I_L} \right|_{\Delta V_s=0} = -R_1/R_2 = -\frac{500 \times 501}{550} = -\frac{500}{11} (\Omega) \checkmark$

$V_o = V_{o1} + V_{o2} = 0.899 + 4.94 = 5.84$
 $(V_s) \quad (V_{z0})$

$V_{o1} = V_s \times \frac{(501/4000)}{500 + (501/4000)} = V_s \times \frac{49.38}{549.38} = 10 \times \frac{49.38}{549.38} = 0.899$

$V_{o2} = V_{z0} \times \frac{(500/4000)}{50 + (500/4000)} = V_{z0} \times \frac{444.44}{494.44} = 5.5 \times \frac{444.44}{494.44} = 4.94$

$\Delta V_o = 5.84 - 5.99 = -0.069$

$-0.069 \times \left(-\frac{11}{500}\right) = 1.518 \text{ mA}$ (a) load regulation: $-\frac{500}{11}$, $\Delta I_L = 1.518 \text{ mA} \checkmark$

A = (b) 負號代表 ΔI_L 與 ΔV_o 為負相關

$\Delta I_L \uparrow \Delta V_o \downarrow \checkmark$

(e)

Zener 無發生

$V_o = 10 \times \frac{500}{500+500} = 5$

$A = V_o = 5V \checkmark$

(f)

Zener 恰發生


$R_L = \frac{V_o}{I_L} = \frac{V_o}{I - I_Z} = \frac{V_o}{\frac{V_o}{R} - I_Z}$

$V_o = 5.5 + 50 \times 0.2 \text{ m} = 5.51$

$R_{L\min} = \frac{5.51}{\frac{5.51}{500} - 0.2 \text{ m}} = \frac{5.51}{6.78 \text{ m}} = 0.813 \text{ k}\Omega \checkmark$

$A = 0.813 \text{ k}\Omega$

2. +8

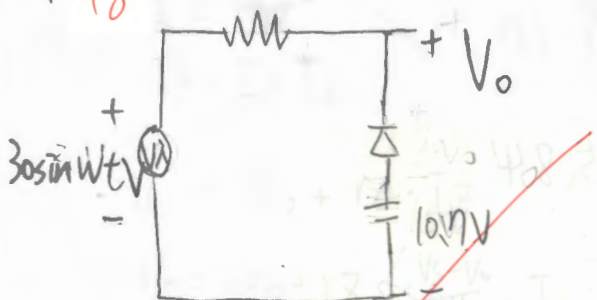

$$V_i = 0 \quad \text{Don} \quad V_o = 10V - 0V = 10V$$

$$V_i < 0 \quad \text{Don} \quad V_o = 10V - 0V = 10V$$

$$V_i \geq 10V - 0V \quad \text{Doff} \quad V_o = V_i$$

3. +3

(a) $D_1, 0\Omega, D_2, 0\Omega$

$$\frac{4.3 - V_A}{2k} + 5mA = \frac{V_A - 0.7 + 5}{2.5k}$$

$$\frac{4.3 - V_A}{2} + 5 = \frac{V_A + 4.3}{2.5}$$

$$2.15 - \frac{V_A}{2} + 5 = \frac{V_A}{2.5} + 1.72$$

$$\frac{9}{10} V_A = 5.43$$

$$V_A = 6.0333 \quad X$$

$D_1, \text{on}, D_2, \text{off}$

$$\frac{5 - 0.7}{2k} = 2.15mA$$

$$I_{D1} = 2.15 + 5 = 7.15$$

$$I_{D1} = 0$$

$$I_{D2} = 5mA$$

$$V_A = 8.2V$$

$$5mA \times 2.5k\Omega$$

$$= 12.5V$$

$$-5 + 12.5 + 0.7$$

$$= 8.2V$$

(b)

$$V_A = 0$$

$$I_{D1} = \frac{5 - 0.7}{2k} = 2.15mA$$

$$I_{D2} = 5 + 2.15mA = 7.15mA$$


$$R = 601\Omega$$

4.
 +4 $(V_1 \text{ and } V_2) \text{ or } (V_3 \text{ and } V_4) \text{ or } V_5$ ✓

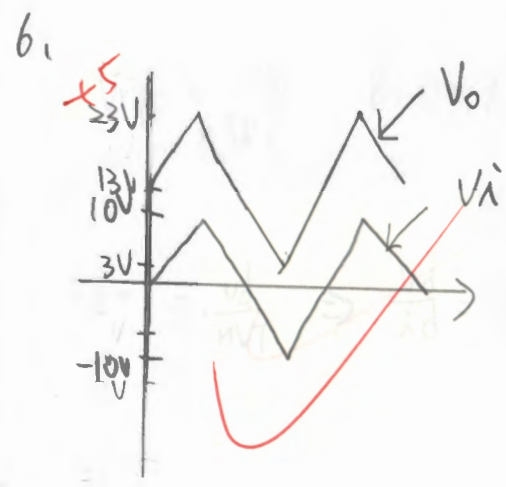5.
 +6 $\frac{16-V}{10k} = I_D + \frac{V}{10k}$
 $I_D = \frac{V-0.7-12}{10k} + \frac{V-0.7}{10k}$
 $\frac{16-V}{10k} = \frac{V-0.7-12}{10k} + \frac{V-0.7}{10k} + \frac{V}{10k}$
 $16-V = V-12.7+V-0.7+V$
 $4V = 16+12.7+0.7$
 $V = 7.35$

$\frac{16-7.35}{10k} = 0.865 \text{ mA}$
 $I_D = 0.865 \text{ mA} - 0.735 \text{ mA} = 0.13 \text{ mA}$

$V_D = 0.7 \text{ V}$
 $A: I_D = 0.13 \text{ mA}$ ✓



7. ⁶ DC AC
 $V_o = (V_s - V_D) + (V_{\hat{\lambda}} - v_d)$
 $= 7.23V + 0.099 \sin(\omega t)$

$$10 - 0.6 - I_D r_f - I_D R = 0$$

$$9.4 - I_D \cdot 130 = 0$$


$$I_D = \frac{9.4}{130} = 72.3 \mu A$$

$$I_D R = 9.4V$$

$$r_d = \frac{2.26 mV}{72.3 \mu A} = 0.72 \Omega$$

$$v_d = \sin(\omega t) \times \frac{100}{100 + 0.72} = 0.099$$
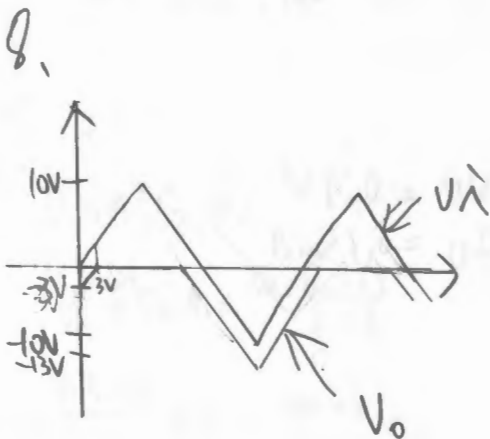
$$A = V_o = 7.23 + 0.099 \sin(\omega t) V$$



$$V_{\hat{\lambda}} = 0, V_o = -3$$

$$V_{\hat{\lambda}} < 0, V_o = -3 + V_{\hat{\lambda}}$$

$$V_{\hat{\lambda}} \geq 3, V_o = 0$$

9. D_1 off, D_2 on, D_3 on

$$V_o = 4.4$$

$$I_{D1} = 0$$

$$I_{D2} = \frac{38-2}{0.5k} = 3.6 mA$$

$$I + I_{D3} = I_{D2}$$

$$\frac{10-4.4}{9.5} + I_{D3} = \frac{38-2}{0.5k}$$

$$I_{D3} = 3.6 - 0.589$$

$$= 3.01$$

A:


$$V_o = 4.4 V$$

$$I_{D1} = 0 mA$$

$$I_{D2} = 3.6 mA$$


$$I_{D3} = 3.01 mA$$

1. filter, 箝位電路, peak circuit

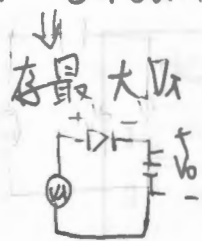

2. diode rectifier \Rightarrow capacitor filter \Rightarrow zener diode regulator

3.

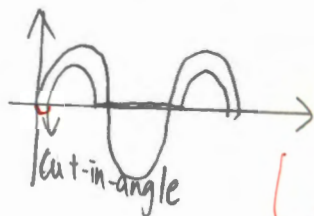

cut-in-angle 代表真正開始產生 V_o 的黑點

4.

$$V_{ripp} = \frac{V_M}{n f R C}$$

固加大電容、電阻或頻率可降低 ripple voltage.

5.

$$\lambda_d = I \cdot \frac{v_d}{nVT} \Rightarrow \frac{v_d}{\lambda_d} = \frac{nVT}{I} = r_d$$

6.

full-wave : $2V_p - V_r$

bridge : $V_p - V_r$

half-wave : V_p